

CS/B.Tech/ECE/Odd/Sem-3rd/EC-301/2014

EC-301

CIRCUIT THEORY AND NETWORKS

Time Allotted: 3 Hours

Full Marks: 70

The questions are of equal value.
The figures in the margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

GROUP A
(Multiple Choice Type Questions)

1. Answer any ten questions.

10 × 1 = 10

- (i) For maximum power to be transferred between the load and the source the condition is
(A) $R_S > R_L$ (B) $R_S = R_L$ (C) $R_S < R_L$ (D) None of these
- (ii) What should be the internal resistance of the ideal voltage source?
(A) 0 (B) ∞ (C) Both (A) and (B) (D) None of these
- (iii) If $f(t) = te^{-2t}$, the Laplace Transform of the function is given by
(A) $\frac{4}{(s+2)^2}$ (B) $\frac{16}{(s+2)^2}$ (C) $\frac{2}{(s+2)^2}$ (D) $\frac{4}{(s+2)}$
- (iv) Superposition Theorem is not applicable to networks having
(A) Transformers (B) Non-linear elements (C) Dependent voltage sources (D) Dependent current sources
- (v) A dc voltage V is applied to a series R-C circuit, the steady state current is
(A) $\frac{V}{R} e^{-t/RC}$ (B) 0 (C) ∞ (D) $\frac{V}{R}$
- (vi) If $f(t)$ and its first derivative is Laplace transformable, then Final value theorem is:
(A) $\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow 0} sF(s)$ (B) $\lim_{t \rightarrow \infty} f(t) = \lim_{s \rightarrow \infty} sF(s)$
(C) $\lim_{t \rightarrow 0} f(t) = \lim_{s \rightarrow 0} sF(s)$ (D) None of these
- (vii) The coefficient of coupling for two coils having $L_1 = 2$ H, $L_2 = 8$ H, $M = 3$ H is
(A) 0.1875 (B) 0.75 (C) 1.333 (D) 5.333

[Turn over]

CS/B.Tech/ECE/Odd/Sem-3rd/EC-301/2014

(viii) A series R-L-C circuit is over damped when

- (A) $R > 2\sqrt{\frac{L}{C}}$ (B) $R < 2\sqrt{\frac{L}{C}}$ (C) $R = 2\sqrt{\frac{L}{C}}$ (D) None of these

(ix) A two port network is reciprocal if and only if

- (A) $z_{11} = z_{22}$ (B) $BC - AD = 1$ (C) $y_{12} = y_{21}$ (D) $h_{12} = h_{21}$

(x) The unit step function of the first derivative of

- (A) ramp function (B) impulse function
(C) gate function (D) parabolic function

(xi) In a series RLC circuit, which of these quality factors have the steepest curve at resonance?

- (A) $Q = 20$ (B) $Q = 12$ (C) $Q = 8$ (D) $Q = 4$

(xii) The graph of a network has six branches with three tree branches. The minimum number of equations required for the solution of the network is

- (A) 2 (B) 3 (C) 4 (D) 5

GROUP B
(Short Answer Type Questions)

Answer any three questions.

3 × 5 = 15

2.

Calculate the node voltages in the circuit (Fig. 1) given below.

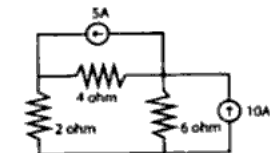


Fig. 1

3.

Draw the oriented graph of the network in the following figure (Fig. 2) and obtain the tie-set matrix.

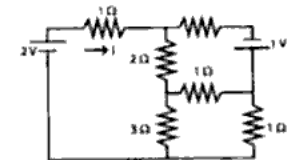


Fig. 2

4.

Find $f(t)$, given that $F(s) = \frac{10s^2 + 4}{s(s+1)(s+2)^2}$

5.

Prove that $AD - BC = 1$.

3054

2

CS/B.Tech/ECE/Odd/Sem-3rd/EC-301/2014

6. In this circuit find the reading of the voltmeter V. Interchange the current source and the voltmeter and verify the reciprocity theorem.

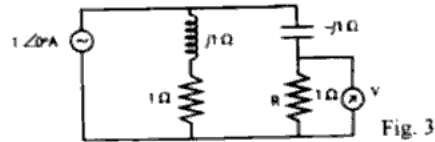


Fig. 3

GROUP C
(Long Answer Type Questions)

Answer any three questions.

3 × 15 = 45

7. a) Calculate the node voltages at nodes 1 and 2 in the following circuit (Fig. 4).

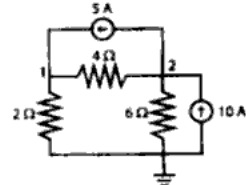


Fig. 4

- b) Find the values of i_1 and i_2 in the following circuit using supermesh analysis (Fig. 5).

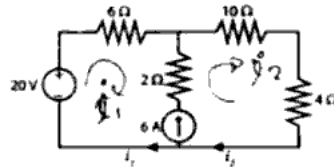


Fig. 5

- c) Find the Norton's equivalent of the circuit shown below (Fig. 6) at terminals a-b.

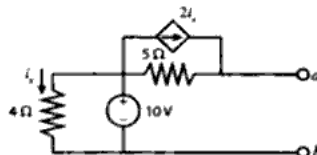


Fig. 6

8. a) State Thevenin's theorem.

- b) Obtain the Thevenin's equivalent of the following circuit (Fig. 7) at terminals a-b.

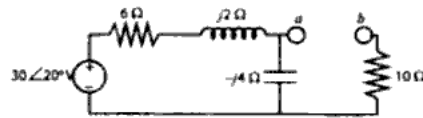


Fig. 7

CS/B.Tech/ECE/Odd/Sem-3rd/EC-301/2014

- c) Apply superposition theorem to find the voltage drop across 0.2 F capacitor in the circuit shown below (Fig. 8).

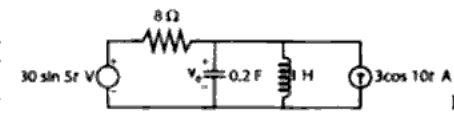


Fig. 8

9. a) Define Laplace transform.

- b) Show that if a function $f(t)$ is piecewise continuous, then the Laplace transform of its derivative is given by $L\left[\frac{df(t)}{dt}\right] = sF(s) - f(0)$ where $F(s) = L[f(t)]$

- c) Find out cut-set matrix from the following graph (Fig. 9).

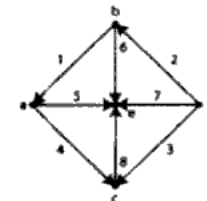


Fig. 9

- d) A series RC circuit consists of a resistor of 10 Ω and a capacitor of 0.1 F. A constant voltage of 20 V is applied to the circuit at $t = 0$. Obtain the current equation. Determine the voltages across the resistor and the capacitor.

10. a) Define the ABCD parameters of a 4-terminal network.

- b) Prove that $AD - BC = 1$.

- c) Derive the symmetry condition for Z-parameters in two port network.

- d) Determine the Z parameters of the following circuit (Fig. 10).

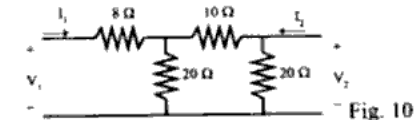


Fig. 10

11. Write short notes on any three of the following:

- Compensation theorem
- Coefficient of coupling
- Hybrid parameters
- Sinusoidal response of series RL circuit.
- Maximum power transfer theorem for complex impedance circuits.