

Name : .....  
Roll No. : .....  
Invigilator's Signature : .....

**CS / B.TECH (ECE) / SEM-4 / EC-402 / 2011**

**2011**

**DIGITAL ELECTRONIC CIRCUITS**

Time Allotted : 3 Hours

Full Marks : 70

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words  
as far as practicable.*

**GROUP – A**

**( Multiple Choice Type Questions )**

1. Choose the correct alternatives for any *ten* of the following :

10 × 1 = 10

i) The Excess-3 representation of decimal 59 is


- a) 01100010                      b) 00111110
- c) 10001100                      d) none of these.

ii) The number of full address required to construct an *m*-bit parallel adder is

- a)  $m/2$                               b)  $m - 2$
- c)  $m$                                   d)  $m + 1$ .



 - iii) The 2's complement representation of  $(-19)_{10}$  is
- a) 101100                      b) 101110
- c) 101101                      d) none of these.
- iv) The maxterm corresponding to decimal 9 is
- a)  $A B' C' D$                       b)  $A + B' + C' + D$
- c)  $A' + B + C + D'$                       d)  $A' B C D'$ .
- v) The number of comparators required in a 8-bit flash type  $A/D$  converter is
- a) 256                              b) 255
- c) 64                                d) 8.
- vi) A 3-bit synchronous counter uses flip-flops with propagation delay of 20 ns each. The maximum possible time required for change of state will be
- a) 60 ns                              b) 40 ns
- c) 20 ns                              d) none of these.



vii) The number of EX-OR gates required for the conversion of 11011 to its equivalent Gray code is

- a) 2
- b) 3
- c) 5
- d) 4.

viii) A mod-2 counter followed by a mod-5 counter is

- a) same as a mod-5 counter followed by a mod-2 counter
- b) a decade counter
- c) a mod-7 counter
- d) none of these.

ix) Which family has better noise margin ?

- a) ECL
- b) DTL
- c) TTL
- d) MOS.

x) The number of *D* flip-flops required to design a mod-10 ring counter is

- a) 5
- b) 10
- c) 9
- d) 8.



xi) A two-input EX-OR gate can be used as an inverter when one of its inputs is kept at logic

- a) 0
- b) 1
- c) either 0 or 1
- d) none of these.

xii) If the resolution of a  $D/A$  converter is approximately 0.4% of its full scale range, it is

- a) an 8-bit converter
- b) a 10-bit converter
- c) a 12-bit converter
- d) a 16-bit converter.

**GROUP – B**

**( Short Answer Type Questions )**

Answer any *three* of the following.  $3 \times 5 = 15$

- 2. Design a Full Adder circuit using a decoder and other necessary logic gates. Assume that the decoder has all active low outputs. 5
- 3. Design a S-R flip-flop with the help of J-K flip-flop. 5
- 4. Implement a 16:1 MUX by using 4 : 1 MUX only. 5




5. a) Distinguish between synchronous and Asynchronous counters. 2
- b) Calculate the frequency of 4-bit ripple counter, if the period of waveform at the last flip-flop is 64 microsecond. 3
6. Design a Binary to Gray code converter using PROM. 5

**GROUP - C**

**( Long Answer Type Questions )**

Answer any *three* of the following. 3 × 15 = 45

 7. a) Design a sequential circuit that implements the following state diagram. (Use D flip-flop) 10



- b) Implement the following Boolean function using 8 : 1 MUX :

$$F(A, B, C, D) = \sum m(0, 7, 8, 9, 10, 11, 15).$$
5



8. a) Design a MOD-6 synchronous up-counter using J-K flip-flops. 7

b) Implement the following function using  $3 \times 4 \times 2$  PLA :

$$F_1(A, B, C) = \sum m(3, 5, 6, 7) \quad F_2(A, B, C) = \sum(0, 2, 4, 7). \quad 8$$

9. a) Simplify the following function in SOP form using Quine MC- Cluskey method :


$$F(A, B, C, D) = \sum m(0, 1, 4, 7, 9, 11, 13, 15) + \sum d(3, 5). \quad 9$$

b) Describe the operation of a two-input NAND gate constructed with CMOS. 6

10. a) Design a combinational circuit for Excess-3 code to BCD conversion using minimum number of logic gates.

9

 b) Describe the principle of operation of successive Approximation type A/D converter. 6



11. Write short notes on any *three* of the following :  $3 \times 5$

- a) 4-bit magnitude comparator
- b) Bi-directional shift register
- c) PAL
- d) Master-slave J-K flip-flop
- e) EEPROM.

=====