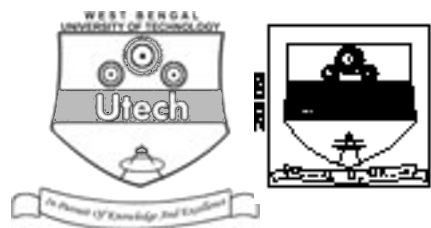


DIGITAL ELECTRONICS & INTEGRATED CIRCUITS (SEMESTER - 4)

CS/B.TECH (EE-N)/SEM-4/EC (EE)-402/09



1.
Signature of Invigilator

2.
Signature of the Officer-in-Charge

Reg. No.

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

Roll No. of the
Candidate

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

CS/B.TECH (EE-N)/SEM-4/EC (EE)-402/09
ENGINEERING & MANAGEMENT EXAMINATIONS, JUNE – 2009
DIGITAL ELECTRONICS & INTEGRATED CIRCUITS (SEMESTER - 4)

Time : 3 Hours]

[Full Marks : 70

INSTRUCTIONS TO THE CANDIDATES :

1. This Booklet is a Question-cum-Answer Booklet. The Booklet consists of **32 pages**. The questions of this concerned subject commence from Page No. 3.
2. a) In **Group – A**, Questions are of Multiple Choice type. You have to write the correct choice in the box provided **against each question**.
b) For **Groups – B & C** you have to answer the questions in the space provided marked 'Answer Sheet'. Questions of **Group – B** are Short answer type. Questions of **Group – C** are Long answer type. Write on both sides of the paper.
3. **Fill in your Roll No. in the box** provided as in your Admit Card before answering the questions.
4. Read the instructions given inside carefully before answering.
5. You should not forget to write the corresponding question numbers while answering.
6. Do not write your name or put any special mark in the booklet that may disclose your identity, which will render you liable to disqualification. Any candidate found copying will be subject to Disciplinary Action under the relevant rules.
7. **Use of Mobile Phone and Programmable Calculator is totally prohibited in the examination hall.**
8. You should return the booklet to the invigilator at the end of the examination and should not take any page of this booklet with you outside the examination hall, **which will lead to disqualification**.
9. Rough work, if necessary is to be done in this booklet only and cross it through.

No additional sheets are to be used and no loose paper will be provided


FOR OFFICE USE / EVALUATION ONLY

Marks Obtained

	Group – A										Group – B					Group – C					Total Marks	Examiner's Signature
Question Number																						
Marks Obtained																						

.....
Head-Examiner/Co-Ordinator/Scrutineer


4526 (10/06)

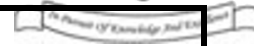

DO NOT WRITE ON THIS PAGE



 ENGINEERING & MANAGEMENT EXAMINATIONS, JUNE – 2009
DIGITAL ELECTRONICS & INTEGRATED CIRCUITS
SEMESTER - 4



Time : 3 Hours]

[Full Marks : 70

GROUP – A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for any *ten* of the following : 10 × 1 = 10

i) The octal equivalent of the binary number 11010111 is

a) 656

b) 327

c) 653

d) D7.

ii) The minimum number of NAND gates required to implement the Boolean function $A + AB' + AB' C$ is equal to

a) zero

b) 1

c) 4

d) 7.

iii) Identify the operation of the following logic gate circuit.

dia

a) OR gate

b) AND gate

c) NOT gate

d) none of these.



iv) The fastest logic gate family is

a) CMOS

b) ECL

c) TTL

d) RTL.



v) The memory, which is ultraviolet erasable and electrically programmable is

a) RAM

b) EEROM

c) EPROM

d) PROM.

vi) A ring counter consists of 5 flip flops will have

a) 5 states

b) 10 states

c) 32 states

d) none of these.

vii) The flip-flop, which is free from race around problem is

a) R-S flip-flop

b) Master-slave JK flip-flop

c) J-K flip-flop

d) none of these.

viii) Identify the carry expression of full adder circuit

a) $X'Y + ZX'$

b) $XY + YZ + ZX$

c) $XY' + YZ' + ZX$

d) $X'Y' + XZ' + YZ.$

ix) Which one is used in EPROM eraser ?

a) Laser light

b) UV ray

c) LED light

d) Sunrays.

x) Gray code of 1011 (binary) =

a) 0101

b) 1101

c) 1110

d) none of these.



5

xi) What is the next octal counting sequence 724, 725, 726, 727?

a) 728

b) 729

c) 730

d) 731.



xii) The equation $\sqrt{(213)} = 13$ is valid for which one of the number system with base ?

a) Base 8

b) Base 6

c) Base 5

d) Base 4.

xiii) A 10 MHz signal is applied to a MOD-5 counter followed by a MOD-8 counter then the o/p frequency will be

a) 10 kHz

b) 2.5 kHz

c) 5 kHz

d) 250 kHz.

xiv) Calculator keyboard is an example of

a) decoder

b) encoder

c) multiplexer

d) demultiplexer.

xv) A single bit memory device is

a) ROM

b) RAM

c) F-F

d) PROM.

GROUP – B

(Short Answer Type Questions)

Answer any *three* of the following questions.

3 × 5 = 15

2. Perform the arithmetic operation :

$$(-22)_{\text{decimal}} + (13)_{\text{decimal}} + (-15)_{\text{decimal}}$$

using 2's complement binary form.



6

3. Minimize the following expression in SOP form using Quine McClusky method :

$$F(A, B, C, D) = \sum m(1, 2, 3, 8, 9, 10, 11, 14) + \sum d(7, 15).$$

4. Explain the race around condition. Draw the Master/Slave JK flip-flop using all NAND gates.

2 + 3

5. Implement a full-adder circuit using 3 to 8 decoder with all active high outputs and other necessary logic gates.

6. Draw and explain the circuit of 8×1 MUX using two 4×1 MUX and one 2×1 MUX.

GROUP – C

(Long Answer Type Questions)

Answer any *three* of the following questions.

$3 \times 15 = 45$

7. a) Design a clocked synchronous sequential network whose state diagram is given below :

8

dia

- b) Design a combinational circuit, which converts excess – 3 number to its corresponding BCD number.

7

8. a) Implement the following Boolean expressions using Decoder.

$$F_1(A, B, C, D) = \sum (1, 2, 5, 7, 8, 10, 12, 13).$$

5

- b) Implement a full adder circuit using minimum number of NOR gates only.

5



- c) An 8 : 1 MUX has inputs A, B, C connected to select line S_2, S_1, S_0 respectively. The data inputs I_0 to I_7 are connected as $I_1 = I_2 = I_7 = 0$, $I_3 = I_5 = 1$, $I_0 = I_4 = D$, $I_6 = D'$. Determine the Boolean expression of the MUX output. 5

9. a) Construct a 4-bit register with parallel load. 10
- b) Describe the basic principles of Successive Approximation Method for A/D converter. 5
10. a) Design MOD-10 synchronous UP-counter using the JK flip-flops and other required logic gates. 10
- b) Calculate the propagation delay for a 4-bit synchronous UP-counter when JK flip-flops are connected in series connection and parallel connection. Given propagation delay t_p (FF) equals to 30 nsec and the propagation delay of the gates used in the circuit are 20 nsec (assumed to be equal for all gates). 5
11. Write short notes on any *three* of the following : 3 × 5
- a) Tri-state gates in TTL family
- b) Data Lock-out in a counter
- c) EPROM
- d) A/D converter
- e) Parity generator.

END