



Name : .....

Roll No. : .....

Invigilator's Signature : .....

**CS/B.Tech(EIE)/SEM-3/EE-301(EI)/2009-10  
2009**

**CIRCUIT THEORY & NETWORKS**

Time Allotted : 3 Hours

Full Marks : 70

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words  
as far as practicable.*

**GROUP – A**

**( Multiple Choice Type Questions )**

1. Choose the correct alternatives for any *ten* of the following :

$$10 \propto 1 = 10$$

- i) If the voltage across a given capacitor is increased, the amount of stored charge
  - a) increases
  - b) decreases
  - c) remains constant
  - d) is exactly doubled.
- ii) A practical voltage source consists of
  - a) an ideal voltage source in series with an internal resistance
  - b) an ideal voltage source in parallel with an internal resistance
  - c) both (a) & (b) are correct
  - d) none of these.



- iii) Determine the current  $I$  in the circuit shown in figure :

Dia.

- a) 2.5 A                                      b) 1A  
c) 3.5 A                                      d) 4.5 A.
- iv) A 1 kHz sinusoidal voltage is applied to an RL circuit. What is the frequency of the resulting current ?
- a) 1 kHz                                      b) 0.1 kHz  
c) 100 kHz                                      d) 2 kHz.
- v) A series circuit consisting of two elements has the following current & applied voltage :

$$i = 4 \cos ( 2000 t + 11.32^\circ ) \text{ A}$$

$$v = 200 \sin ( 2000 t + 50^\circ ) \text{ V}$$

The circuit elements are

- a) resistance & capacitance  
b) capacitance & inductance  
c) inductance & resistance  
d) both resistances.
- vi) In a certain RL circuit,  $V_R = 2 \text{ V}$  &  $V_L = 3 \text{ V}$ .

What is the magnitude of the total voltage ?

- a) 2 V                                      b) 3 V  
c) 5 V                                      d) 3.61 V.
- vii) Maximum power transfer occurs at
- a) 100% efficiency                      b) 50% efficiency  
c) 25% efficiency                      d) 75% efficiency.



- viii) A source has an emf of 10V and impedance of  $500 + j100\Omega$ . The amount of maximum power transferred to the load will be
- a) 0.5 mW                                      b) 0.05 mW  
c) 0.05 W                                        d) 0.5 W.
- ix) Transient current in an RLC circuit is oscillatory when
- a)  $R = 2\sqrt{L/C}$                                       b)  $R = 0$   
c)  $R > 2\sqrt{L/C}$                                       d)  $R < 2\sqrt{L/C}$  .
- x) When a series RL circuit is connected to a voltage V at  $t = 0$ , the current passing through the inductor L at  $t = 0^+$  is
- a)  $\frac{V}{R}$     b) infinite  
c) zero    d)  $\frac{V}{L}$  .
- xi) The current in the neutral wire of a balanced three-phase, four-wire star-connected load is given by
- a) zero  
b)  $\sqrt{3}$  times the current in each phase  
c) 3 times the current in each phase  
d) the current in each phase.
- xii) A two port network is simply a network inside a black box & the network has only
- a) two terminals  
b) two pairs of accessible terminals  
c) two pairs of ports  
d) 4 pairs of ports.



**GROUP – B**

**( Short Answer Type Questions )**

Answer any *three* of the following.

$$3 \times 5 = 15$$

2. Determine the voltage  $V$  which causes the current  $I_1$  to be zero in the circuit shown Use mesh analysis.

Dia.

3. A series circuit consisting of two pure elements has the following current & voltage :

$$v = 100 \sin ( 2000 t + 50^\circ ) V$$

$$i = 20 \cos ( 2000 t + 20^\circ ) A$$

Find the element in the circuit.

4. A three phase balanced delta-connected load with line voltage of 200 V, has line currents as  $I_1 = 10 \angle 90^\circ$ ,

$$I_2 = 10 \angle -150^\circ \text{ \& } I_3 = 10 \angle -30^\circ.$$

- a) What is the phase sequence ?  
b) What are the impedances ?



5. For the circuit shown in figure, find the complete expression for the current when the switch is closed at  $t = 0$  :

dia.

6. Find the Norton's equivalent circuit across terminal  $AB$  for the circuit shown.

Dia.

### GROUP – C

#### ( Long Answer Type Questions )

Answer any *three* of the following.  $3 \times 15 = 45$

7. a) The circuit shown in figure consists of series  $R - L$  elements. The sine wave is applied to the circuit when the switch  $S$  is closed at  $t = 0$ . Determine the current  $i(t)$

Dia.



- b) Find the Laplace transform of the waveform shown :

Dia.

10 + 5

8. a) For the parallel circuit shown in figure. Find the magnitude of current in each. Branch & the total current. What is the phase angle between the applied voltage & current ?


Dia.

- b) Two impedances  $Z_1 = 20 + j 10$  &  $Z_2 = 10 - j 30$  are connected in parallel & this combination is connected in series with  $Z_3 = 30 + j X$ . Find the value of  $X$  which will produce resonance.

9 + 6

9. a) Find Z-parameters of the network shown in figure. Hence find the ABCD parameters for the same network.

Dia.

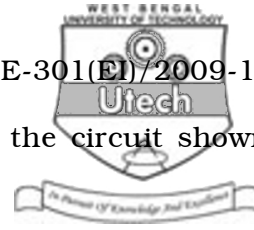

- b) Calculate the effective inductance of the circuit shown in figure

Dia.

10 + 5


10. a) Determine the load resistance to receive maximum power from the source. Also find the maximum power delivered to the load in the circuit shown.

Dia.

- b) Determine the output voltage  $V_{\text{out}}$  in the circuit shown.

Dia.

9 + 6

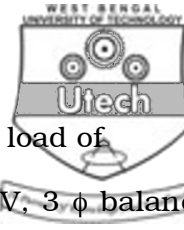

11. a) A three phase, balanced delta connected load of  $(4 + j8) \Omega$  is connected across a 400 V, 3  $\phi$  balanced supply. Determine the phase currents & line currents. Assume the phase sequence to be RYB. Also calculate the power drawn by the load.
- b) Calculate the total power input & readings of the two wattmeters connected to measure power in a three phase balanced load if the reactive power input is 15 kVAR & load p.f. is 0.8.
- 10 + 5

=====