



Name : .....

Roll No. : .....

Invigilator's Signature : .....

**CS/B.TECH (EIE-N)/SEM-3/EE(EI)-301/2011-12**

**2011**

**CIRCUIT THEORY & NETWORKS**

Time Allotted : 3 Hours

Full Marks : 70

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words  
as far as practicable.*


**GROUP – A**

**( Multiple Choice Type Questions )**

1. Choose the correct alternatives for any *ten* of the following :

$$10 \times 1 = 10$$

- i) A circuit has 5 branches, 4 nodes and no separate parts. The number of independent mesh equations is
  - a) 1
  - b) 2
  - c) 3
  - d) 5.
- ii) A notch filter is basically a
  - a) low-pass filter
  - b) high-pass filter
  - c) band-pass filter
  - d) band-reject filter.
- iii) A capacitor  $C$  at time  $t = 0 +$  with zero initial charge acts as a
  - a) short circuit
  - b) open circuit
  - c) current source
  - d) voltage source.

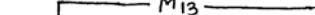- 
 $L_1 = 1\text{H}, L_2 = 2\text{H}, L_3 = 5\text{H}$   
 $M_{12} = 0.5\text{H}, M_{13} = 1\text{H}$   
 $M_{23} = 1\text{H}$

- 2

- ### GROUP – B

Answer any *three* of the following.

Answer any *three* of the following.


- $$x'' + 3x' + 2x = 0 ;$$

$$x'(0) = 4, x(0) = 0$$


- 3108-(N)



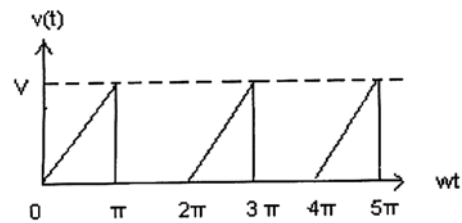
4. Find the trigonometric Fourier series for the waveform shown in the following figure and sketch the spectra :



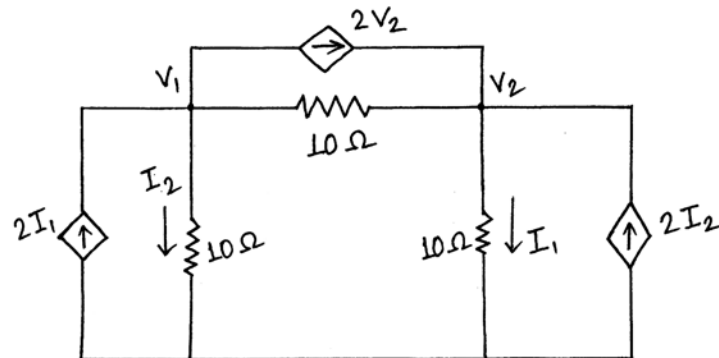5. Find the voltages  $V_1$  and  $V_2$  at the node.



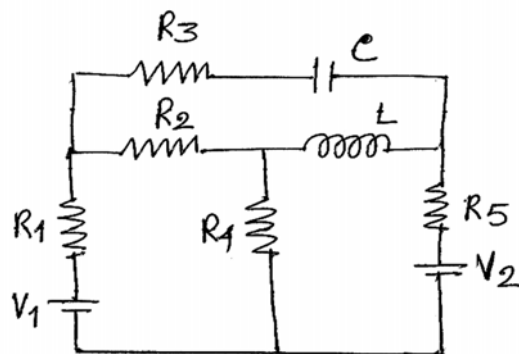6. Draw a connected, planar graph for the circuit given below. Obtain the reduced incidence matrix for the graph. 3 + 2






**GROUP – C**


**( Long Answer Type Questions )**

Answer any *three* of the following.  $3 \times 15 = 45$

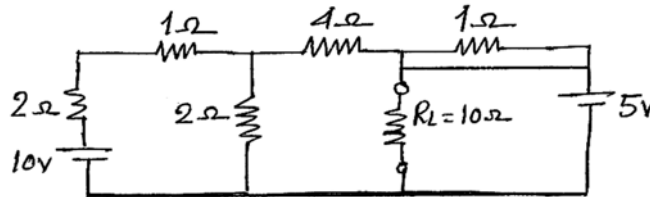7. a) State Thevenin's theorem. 2
- b) Use Thevenin's theorem to determine the load current in the circuit given below : 7



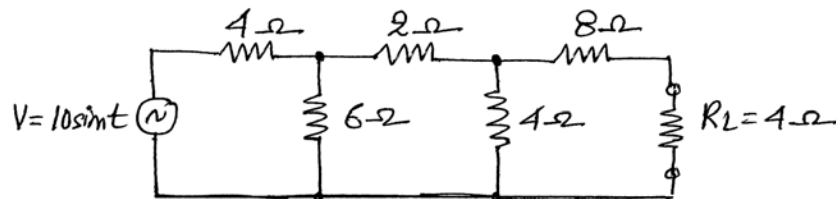
- c) Find the maximum power delivered to the load in the circuit given below : 6




8. a) Draw the circuit diagram of a first order high-pass filter and find out the expression of the cut-off frequency. 5
- b) Draw and explain the characteristics of ideal band-pass and band-stop filters. 5



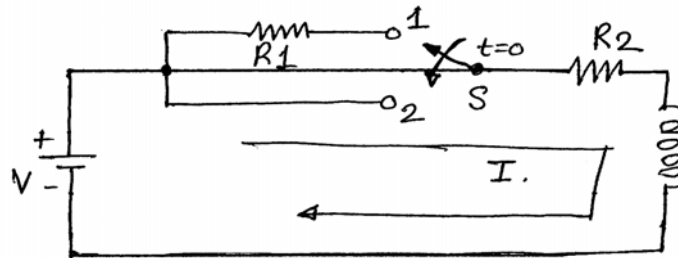- c) In the circuit shown below, the switch 'S' is thrown to position 1 for a long period of time. Find the complete expression for the current 'I' after throwing the switch 'S' to position 2 which removes  $R_1$  from the circuit. 5



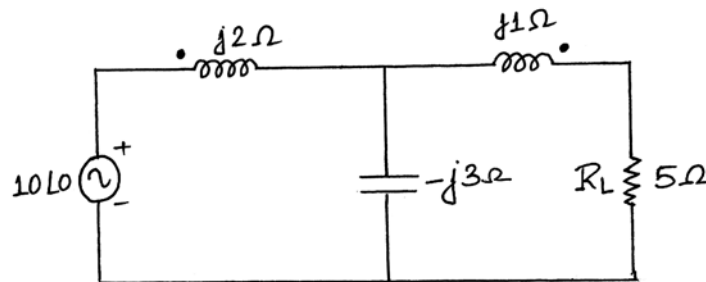
9. a) Consider two coupled coils with flux value as  $\phi_{11} = 0.5 \text{ mWb}$ ,  $\phi_{12} = 0.3 \text{ mWb}$ . The number of turns in the first and second coils are 100 and 500 respectively. Find,
- coefficient of coupling (K)
  - inductances  $L_1$  and  $L_2$
  - mutual inductance (M)
- b) Find the voltage drop across RL. (Coefficient of coupling,  $K = 0.5$ )



- c) Give two examples each for linear and non-linear circuit elements. 2



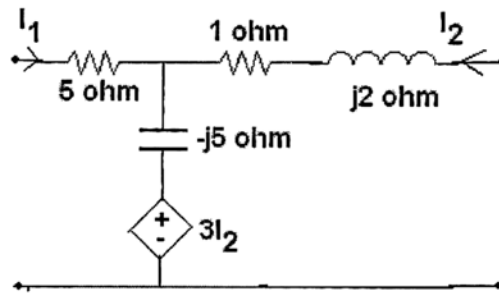10. a) Find the Z-parameters and ABCD parameters of the circuit given below : 8



- b) Express  $h$ -parameters in terms of Y-parameters of a two-port network. 4
- c) What is the cascade connection between two 2-port networks ? Explain with diagram. 3
11. a) Explain two-wattmeter method for three phase power measurement. 5
- b) A balanced star-connected load with impedances of  $20 \angle -30^\circ$  ohms is supplied from 3 phase, 4 wire, 170/100 volt system, the voltages to neutral being  $V_{AN} = 100 \angle 150^\circ$ ,  $V_{BN} = 100 \angle 30^\circ$ ,  $V_{CN} = 100 \angle 270^\circ$  volts. Determine the currents in the line conductors and the current in the neutral. Draw the relevant circuit and phasor diagrams. 10

=====