ELECTRONIC INSTRUMENTATION & MEASUREMENT (SEMESTER - 6)

CS/B.TECH (EIE-NEW)/SEM-6/EI-603/09						© Utech										
1.	Signature of Invigilator									~~		2111				
2.	Signature of the Officer-in-Charge	g. No														
	Roll No. of the Candidate															
	CS/B.TECH ENGINEERING & MA	NAGI	E M I	ENT	EX	AM	INA	TIC	NS	, Jt	JNE					
	ELECTRONIC INSTRUMEN	TAT	Oľ	N 8	k M	EA	SUI	RE	ME	NT	' (S	EN				•
Tin	ne : 3 Hours]												[Fu	ıll M	Iark	s:70
	STRUCTIONS TO THE CANDIDA						_									
1.	This Booklet is a Question-cum-And concerned subject commence from F				The I	3ook	let c	onsi	sts	of 32	pag	ges.	The q	uest	ions	of this
2.	a) In Group - A , Questions are provided marked 'Answer St	of Mu			oice 1	type.	You	hav	e to	writ	e the	cor	rect c	hoice	e in t	he box
	b) For Groups – B & C you h Sheet'. Questions of Group - type. Write on both sides of t	- B ar	e S													
3.	Fill in your Roll No. in the box pro			n you	ır Ad	mit	Card	bef	ore a	answ	ering	g the	ques	tions	١.	
4.	Read the instructions given inside carefully before answering.															
5.	You should not forget to write the corresponding question numbers while answering.															
6.	Do not write your name or put any render you liable to disqualification under the relevant rules.															
7.	Use of Mobile Phone and Programs	mable	Cal	cula	tor is	s tot	ally	pro	hibi	ted i	n th	e ex	amin	ation	hal	l.
8.	You should return the booklet to the	You should return the booklet to the invigilator at the end of the examination and should not take any page of this booklet with you outside the examination hall, which will lead to disqualification .														
9.	Rough work, if necessary is to be do:											1				
	No additional sheets are										_	pro	video	1		

FOR OFFICE USE / EVALUATION ONLY Marks Obtained

Group - A Group - B Group - C

Guestion Number Marks
Obtained Group - B Group - C

Group - B Group - C


Total Examiner's Marks Signature

Head-Examiner,	/Co-Ordinator	/Scrutineer

6846 (15/06)





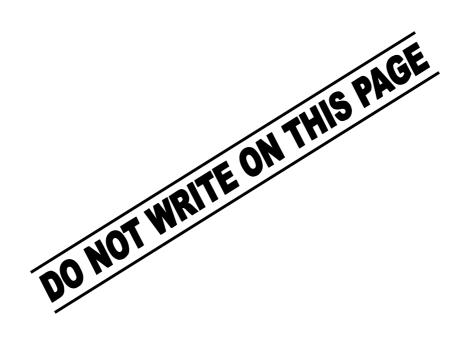

ENGINEERING & MANAGEMENT EXAMINATIONS, JUNE – 2009 ELECTRONIC INSTRUMENTATION & MEASUREMENT SEMESTER – 6

Time: 3 Hours]

Full Marks : 70

GROUP - A

(Multiple Choice Type Questions)

1.	Choo	Choose the correct alternatives for any <i>ten</i> of the following :									
	i)	In a phase lock loop,									
		a)	capture range is smaller than lock range								
		b)	lock range is smaller than capture range								
		c)	capture range is equal to lock range								
		d)	none of these.								
	ii)	Spectrum analyzer is used across the frequency spectrum of a given signal study the									
		a)	current distortion	b)	voltage distortion						
		c)	energy distortion	d)	power distortion.						
	iii)	What type of noise is found in semiconductor devices?									
		a)	Shot noise	b)	Thermal noise						
		c)	Johnson noise	d)	None of these.						
	iv)	In a ballistic galvanometer, damping follows									
		a)	hyperbolic decay	b)	exponential decay						
		c)	logarithmic decay	d)	exponential rise.						



- A thermocouple ammeter is used to measure a 10 MHz sine wave and it indicates v) a current of 2 A in a pure resistance. The peak current in this waveform is
 - 2 A a)

0.2 A b)

2.83 A c)

- If V_c is the control d.c. voltage and V+ is the supply voltage, then the frequency of vi) oscillation of a VCO is
 - $(1/R_1C_1)\{(V^+-V_c)/V^+\}$
- b) $(2/R_1C_1)\{(V^+ V_c)/V^+\}$
- c)
- $(2/R_1C_1)\{(V^+ V_c)/V_c\}$ d) $(1/R_1C_1)\{(V^+ V_c)/V_c\}$.
- The commonly used PLL chip is vii)
 - a) NE 500

b) LM 522

NE 565 c)

- NE 465. d)
- If the distance of screen from a CRT to center of deflection plates is 15 cm. The viii) length of deflection plates is 2 cm, the distance between plates is 1 cm and the accelerating voltage is 500 Volt, the deflection sensitivity is
 - 33.2 volt/cm a)

0.03 cm/volt b)

66.4 volt/cm c)

- 0.015 cm/volt. d)
- A differential amplifier has a common mode gain of 0.02. It has +200m V signals ix) applied to each of the inputs. The amplitude of output signal is
 - 0 V a)

8 mV b)

c) 4 mV

- none of these. d)
- The true value of Q of coil is 245 and the measured value of 244.5. The ratio of X) distributed capacitance to self-capacitance of the coil is
 - 2.04×10^{-3} a)

b) 1.002

0.997 c)

none of these. d)

d)



- xi) Bolometer is used to measure
 - a) power

b) frequency

c) temperature

- current.
- xii) Operating temperature range of a LCD is
 - a) wide, 0-70 degree centigrade
 - b) restricted, 10-30 degree centigrade
 - c) more than 70 degree centigrade
 - d) restricted, less than 10 degree centigrade.

GROUP - B

(Short Answer Type Questions)

Answer any *three* of the following questions.

 $3 \times 5 = 15$

- 2. a) What is a current mirror?
 - b) Draw the circuit diagram of current mirror circuit and explain the operating principle. 1+1+3
- 3. A saw tooth voltage has a peak value of 160 V and a time period 3.6 sec as shown in following fig. Calculate the error when measuring the voltage with an average reading voltmeter calibrated in terms of *rms* value of a sinusoidal wave.



4. What is Chopper Amplifier? How does it work for D.C. amplification?

1 + 4

With diagram, explain the operation of a charge amplifier connected to a piezoelectric transducer.

- 6. a) What is noise?
 - b) What are the different types of noise?
 - c) Derive the expression of thermal noise in a resistor.

2 + 1 + 2

GROUP - C

(Long Answer Type Questions)

Answer any *three* of the following questions.

 $3 \times 15 = 45$

- 7. a) What is the operating principle of LCD display?
 - b) What are the advantages of LCD display over LED display?
 - c) Explain why reflective LCDs have many advantages over transmissive LCDs.
 - d) Explain with the help of a neat diagram, the working of Digital Frequency Meter. 4+4+4+3
- 8. a) Define the Q-factor of a coil. Explain with a circuit diagram, the construction and principle of operation of a basic Q-meter.
 - b) To find the self capacitance of a coil by *Q*-meter, the resonance was obtained with
 - i) tuning capacitor of 1530 pF at 1.0 MHz and
 - ii) tuning capacitor of 162 pF at 3.0 MHz.
 - c) What are the errors present in *Q*-meter?

1 + 7 + 4 + 3



- 9. a) What will effect for a phase-detector of a PLL when a square wave input is given to it? Explain with relevant circuit and timing diagrams.
 - b) How is a Digital Frequency Meter used for ratio measurement?
- 10. Explain with a neat block diagram, the operation of a superheterodyne spectrum analyzer. Explain the frequency instabilities and dynamic range of a spectrum analyzer. Calculate the dynamic range of a spectrum analyzer with a third order intercept point of 20 dBm and a noise level of 100 dBm. 7+3+3+2
- 11. a) Explain the operation of a dual-slope integrating type digital voltmeter. How does range changing circuit work for a DVM?
 - b) Draw the circuit for a FET-input voltmeter using dual emitter follower and an input attenuator.
 - c) Determine the meter reading of a FET input voltmeter, when E = 7.5 V and the meter is set to its 10 V range. The FET gate-source voltage is -5 V.

$$V_p = +5 \text{ V}$$
, Rs + Rm = 1 k Ω and Im = 1 mA at full scale. $7 + 3 + 5$

END