



**MAULANA ABUL KALAM AZAD UNIVERSITY OF
TECHNOLOGY, WEST BENGAL**

Paper Code : ES-201

**BASIC ELECTRICAL & ELECTRONIC
ENGINEERING - II**

Time Allotted : 3 Hours

Full Marks : 70

*The figures in the margin indicate full marks.
Candidates are required to give their answers in their own
words as far as practicable.*


PART - I (Electrical)

GROUP - A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for any *five* of the following : 5 × 1 = 5
- i) Iron losses in a dc machine are independent of variation in
- | | |
|--------------|------------------|
| a) frequency | b) load |
| c) voltage | d) flux density. |
- ii) A series motor will run at very high speed when
- | |
|---------------------------|
| a) the load is increased |
| b) the field is opened |
| c) the armature is opened |
| d) the load is removed. |

- iii) A transformer core is laminated to
- | |
|---------------------------------------|
| a) reduce hysteresis loss |
| b) reduce eddy current loss |
| c) reduce copper losses |
| d) reduce all losses mentioned above. |
- iv) The effective capacitance between terminals A & B is given by

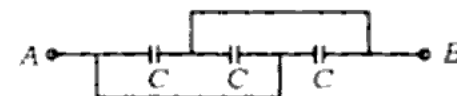

- | | |
|-------|---------|
| a) 2C | b) 3C |
| c) C | d) C/3. |
- v) In a 3-phase balanced system, the line voltage makes an angle with phase voltage. The value of the angle is
- | | |
|--------|----------|
| a) 30° | b) 60° |
| c) 90° | d) 120°. |
- vi) If the induction motor is supplied with voltage having frequency f and s is the slip of the motor, then the frequency of rotor current is given by
- | | |
|-------------|---------------|
| a) sf | b) f |
| c) $sf + f$ | d) $sf - f$. |

GROUP - B


(Short Answer Type Questions)

Answer any *two* of the following. 2 × 5 = 10

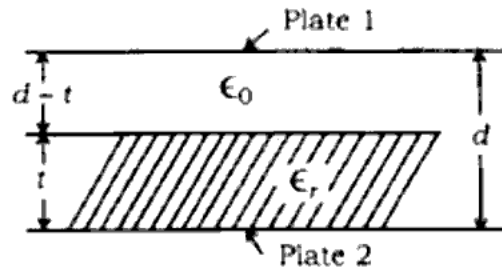2. Show that if a dielectric of thickness t and with the same area as the plates of parallel plate capacitor is

introduced, the capacitor would then have the

$$\text{capacitance } C = \frac{\epsilon_0 A}{d - t \frac{t}{\epsilon_r}}$$



3. A star connected three-phase load draws a current of 15A at a lagging power factor of 0.9 from a balanced 440 V, 50 Hz supply. Find the circuit elements in each phase of the elements connected in series.
4. What do you mean by the term 'back emf'? Derive the expression of torque of a separately excited dc motor. 1 + 4
5. Explain the working of a transformer on load.

GROUP - C

(Long Answer Type Questions)

Answer any two of the following. 2 × 10 = 20

6. a) Explain why the open circuit test on a transformer is conducted at a rated voltage.
- b) The following test data were obtained on a 20 kVA, 50 Hz, 1 ph, 2000/200 V transformer.
 No. load test : 200 V, 1 A, 120 W
 Short circuit test : 60 A, 10 A, 300 W.
 Find —
 - i) efficiency of the transformer at $\frac{1}{2}$ of the full load and 0.8 p.f. lagging.
 - ii) maximum efficiency and the load at which it occurs. 2 + 8

7. a) What is commutation in a dc machine ?
- b) A 4-pole 240 V dc shunt motor has armature and shunt field resistances of 0.24 Ω and 240 Ω respectively. It takes 20 A from a 240 V dc supply while running at a speed of 1000 rpm. Find —
 - (i) field current, (ii) armature current, (iii) back emf, (iv) torque developed in Nm. 2 + 8
8. a) Derive the exact equivalent circuit of a 3-phase induction motor on per phase basis.
- b) Discuss voltage control method of speed control of induction motor. 5 + 5
9. Write short notes on any two of the following : 2 × 5
 - a) Speed control of dc motor by armature voltage control
 - b) General single line diagram of an electrical power system from power generation to distribution
 - c) Torque-speed characteristics of a 3-phase induction motor
 - d) 3-point starter.

PART - II (Electronics)
GROUP - A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for any *five* of the following : 5 × 1 = 5
- i) JFET is a
- voltage controlled voltage source
 - voltage controlled current source
 - current controlled voltage source
 - current controlled current source.
- ii) When the gate source voltage of N-channel JFET is more negative, the drain current
- increases
 - decreases
 - remains constant
 - may increase or decrease.
- iii) $|AB| = 1$
- sustained oscillations
 - exponentially decay
 - exponentially increased
 - none of these.
- iv) Which of the following statements is/are correct in regard to excess 3 codes ?
- It is a BCD code
 - It is an unweighted code
 - It is a self-complementing code
 - All of these.
- v) In inverting amplifier circuit if input feedback resistances are 1 k Ω and 2 k Ω respectively, i/p voltage is 3 V and power supply voltage is $\pm 6V$, then the o/p voltage of an Op-Amp is
- | | |
|--------|---------------|
| a) -6V | b) +6V |
| c) -9V | d) $\pm 9V$. |


- vi) The minimum number of 2-input NAND gates required to implement the XOR operation of 2 variables is
- | | |
|------|-------|
| a) 5 | b) 4 |
| c) 6 | d) 2. |

GROUP - B

(Short Answer Type Questions)

Answer any *two* of the following. 2 × 5 = 10

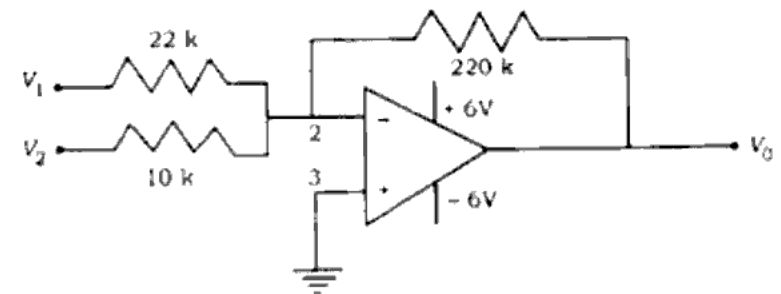- Why do p-channel enhancement mode MOSFETs require threshold voltage ? Explain with suitable diagram.
- What is oscillator ? Which type of feedback is used to design an oscillator ? Draw the block diagram of an oscillator and explain its principle of operation. 1 + 1 + 3
- Identify the circuit and calculate the output voltage when $V_1 = 350$ mV and $V_2 = 200$ mV. 1 + 4



- Perform the following number conversions :
 - $(456)_{16} = (?)_8$
 - $(1010101)_2 = (?)_{16}$
 - Realize the Boolean expression using minimum number of NAND gates :

$$Y = (A + \bar{B})(\bar{A} + B)$$
3 +

CS/B.TECH/EVEN/SEM-2/ES-201/2015-16

GROUP - C

(Long Answer Type Questions)

Answer any *two* of the following. $2 \times 10 = 20$

6. a) Explain the basic operation of n-channel JFET with suitable diagram.
b) What are the differences between MOSFET and JFET ?
c) An n-channel JFET has $I_{DSS} = 12$ mA and pinch-off voltage is -4 V, find the I_D for $V_{GS} = -2$ V. If the g_{mo} of a JFET with same L_{DSS} at $V_{GS} = 0$ is 4 millimho, find pinch-off voltage. $4 + 2 + 4$
7. a) What is negative feedback ? Draw the block diagram of different types of feedback topologies.
b) An amplifier has a voltage gain of -100 . The feedback ratio is -0.04 . Find (i) voltage gain with feedback, (ii) amount of voltage gain, (iii) the output voltage of the feedback amplifier for an input voltage of 40 mV. $2 + 4 + 4$
8. a) Write down De Morgan theorem.
b) Perform the following number conversion :
i) $(11001 \cdot 101)_2 = (?)_8$
ii) $(284 \cdot 56)_{10} = (?)_2$
c) Realize the Boolean expression using basic gates.
 $Y = B(\overline{AC} + \overline{AC}) + A\overline{BC}$ $2 + 4 + 4$
9. Write short notes on any *two* of the following : 2×5
a) Summing Amplifier
b) CMOS
c) Different parameters of JFET
d) Race around condition in JK latch.