



Name : .....

Roll No. : .....

Invigilator's Signature : .....

**CS/B.TECH (EEE/ICE) (OLD)/SEM-4/EC-401/2012**

**2012**

**ANALOG ELECTRONIC CIRCUITS**

*Time Allotted : 3 Hours*

*Full Marks : 70*

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words  
as far as practicable.*

**GROUP – A**

**( Multiple Choice Type Questions )**

1. Choose the correct alternatives for the following :

$10 \times 1 = 10$

- i) Damping factor of second order Butterworth filter is
  - a) 1.73                                      b) 1.414
  - c) 1.06                                      d) 0.5.
- ii) The input offset voltage in an Op-Amp is due to
  - a) mismatch in transistor parameters
  - b) voltage irregularity
  - c) imperfect ground
  - d) none of these.

4030 (O)

[ Turn over



iii) If gain is  $A$  and feedback factor is  $\beta$ , then condition to sustain oscillation of Wein-bridge oscillator is

- a)  $A = 1/3, \beta = 3$
- b)  $A = 3, \beta = 1/3$
- c)  $A = 6, \beta = 1/6$
- d)  $A = 1/6, \beta = 6.$

iv) The current in FET is

- a) only due to minority carriers
- b) only due to majority carriers
- c) due to both
- d) none of these.

v) Commercially available Op-Amp is

- a) IC 742                                      b) IC 723
- c) IC 741                                      d) IC 555.

vi) The temperature coefficient of the Zener breakdown voltage is

- a) positive                                      b) negative
- c) zero    d) none of these.



vii) The CMRR of an Op-Amp is

- a) much larger than unity
- b) zero
- c) much smaller than unity
- d) unity.

viii) A BJT can act as a switch, when it changes from

- a) cut-off to active region
- b) active to saturation
- c) forward active mode to reverse active mode
- d) saturation to cut-off region.

ix) For an enhancement mode  $n$ -MOSFET, the threshold voltage is

- a) positive
- b) negative
- c) zero
- d) none of these.

x) Maximum efficiency of class  $B$  push-pull power amplifier is

- a) 25%
- b) 65%
- c) 78.5%
- d) 95%.



**GROUP - B**

**( Short Answer Type Questions )**

Answer any *three* of the following.  $3 \times 5 = 15$

2. Draw a circuit of a class *B* push-pull power amplifier. Derive its maximum power efficiency and collector dissipation.  $2 + 3$
3. a) Obtain the expression for output voltage of an integrator using Op-Amp.  
  
b) Draw the output waveforms if input of a differentiator is
  - i) Triangular wave
  - ii) Sine wave.  $2 + 3$
4. Show that depletion width ( *W* ) of a *p-n* junction diode is related to applied potential *V* in the following way :  
$$W \propto K \sqrt{V_0 - V}$$
 where, *K* is a constant and *V*<sub>0</sub> is the contact potential.  $5$
5. What are the differences between series and shunt regulators ? Draw a circuit of a shunt regulator and explain its operation.  $2 + 3$
6. What do you mean by clamping circuit ? Draw its circuit diagram and discuss its operation.



**GROUP – C**

**( Long Answer Type Questions )**

Answer any *three* of the following.  $3 \times 15 = 45$

7. a) Sketch the basic structure of an  $n$ -channel enhancement type MOSFET and explain the various parts of it.
- b) How does the name enhancement and depletion type MOSFET comes into picture ?
- c) Show the circuit symbol for both enhancement and depletion type  $n$ -channel MOSFET.
- d) Draw the  $i_D - V_{DS}$  characteristic curve for common source configuration and indicate all the three regions of operation.  $4 + 6 + 2 + 3$
8. a) What are the characteristics of Ideal Op-Amp ? Establish the relationship between slew rate and full power bandwidth.
- b) Design a circuit to implement the function  $f = 3x + \log(2x) + \sin 4x$ .
- c) Why hysteresis is desirable in a Schmitt Trigger Circuit ?
- d) Why multipliers are used for operation of TV picture tube voltage rather than transformers ?

$3 + 4 + 4 + 2 + 2$



9. a) Draw the Eber's Moll model of the *pnp*-transistor and give the equations for the emitter current and collector current. 5

b) Define and describe about LED. 5

c) Draw the small-signal high-frequency *CE* model of a transistor. How does  $g_m$  vary with  $|I_C|$ ,  $|V_{CE}|$  and  $|T|$ ? 2 + 3

10. Write short notes on any *three* of the following : 3 × 5

- a) Wien Bridge Oscillator
- b) Four basic feedback topologies
- c) Astable multivibrator
- d) Spice model of MOSFET
- e) Active Filter.



11. a) What do you mean by feedback in amplifiers ? 2
- b) Derive an expression for the closed-loop gain of the amplifier with feedback. 6
- c) State the assumptions made in your derivation. 3
- d) Write down the effect of negative feedback in an amplifier in terms of gain, bandwidth, input resistance and output resistance with respect to voltage series configuration. 4
-