	Uneah
Name:	
Roll No.:	To Stampe (I' Executing 2nd Exellent
Invigilator's Signature :	•••••

CS/M.TECH (CT)/SEM-1/M(CT)-105/2010-11 2010-11

ELECTRONIC INSTRUMENTATION

Time Allotted: 3 Hours Full Marks: 70

The figures in the margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

Answer any *five* questions. $5 \propto 14 = 70$


- 1. a) What is the function of ammeter? Explain with diagram the working principle of a moving iron ammeter. 1 + 5
 - b) What is the basic difference between moving iron and moving coil based meters?
 - c) A moving coil ammeter reads upto 10 amperes when it has a resistance of 0.2 ohm. How the ammeter can be used to read current up to 100 amperes?

40305 [Turn over

CS/M.TECH (CT)/SEM-1/M(CT)-105/2010-11

		<u>Uffech</u>
2.	a)	What are the properties used for an electronic voltmeter?
	b)	Explain the working principle of an electronic meter
	D)	with diagram.
	c)	What is watt-hour-metre? 2
	d)	Why is LCR meter used?
3.	a)	What is the purpose of an oscilloscope? 3
	b)	Describe the working principle of an oscilloscope with block diagram.
	c)	Describe the function of control grid of a Cathode Ray Tube. 3
4.	a)	Describe SAR method of A/D conversion with diagram.
		6
	b)	Describe with diagram a 4-bit D/A converter. 5
	c)	What is shift register and why are they used? 3
5.	a)	What are the types of flip-flops ? Describe any one flip-flop. $2+5$
	b)	What are the features of an Op-Amp?
	c)	How an Op-Amp can be used as voltage comparator? 4
6.	a)	What is seven segment display and how the segments can be illuminated of a seven segment display using decoder? $2+5$
	b)	What is the function of a Decade Counter? Describe a
		Decade Counter with diagram. 2 + 5

40305 2

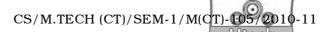

- 7. a) Describe the basic elements of a Microprocessor based system.
 - b) What are the features of a Microcontroller?
 - c) Justify the uses of Microprocessor based system andMicrocontroller based system.5
- 8. Describe with diagram the Microprocessor based Temperature Controller of a furnace.

40305 3 [Turn over