



Name :

Roll No. :

Invigilator's Signature :

CS/M.Tech(ECE)/SEM-1/MVLSI-103/2012-13

2012

DIGITAL IC DESIGN

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

GROUP – A

(Objective Type Questions)

1. Answer any *five* of following : 5 × 2 = 10

- a) Draw the layout of 2 input and gate.
- b) Draw a 1 bit full adder using dynamic logic.
- c) Write the program of master slave flip-flop using VHDL.
- d) What is bootstrap capacitance ?
- e) Draw the symbols of inverter, AND, OR, XOR gates in BDD.
- f) How the following Boolean function can be realized with TG.

$$F = A + BC$$



GROUP - B
(Short Answer Type Questions)

Answer any *three* of the following.

3 × 5 = 15

2. Describe the operation (Read and write) of 1bit SRAM Cell.
3. Write the program of parity generator using VHDL code.
4. What are the rules for layout ? Draw the layout for 1bit full adder.
5. Draw the circuit diagram of a dynamic shift register with enhancement load and explain its operation.
6. Design the state diagram for handshaking mechanism of a communication system.

GROUP - C
(Long Answer Type Questions)

Answer any *three* of the following.

3 × 15 = 45

7.
 - a) How many types of VHDL programming are there ?
 - b) Design a seven segment display to glow 2012 and write down its program in VHDL.
8.
 - a) What is logic optimization ? Why is it needed ?
 - b) Design a mod 10 counter using an optimized logic method and justify your chosen method.

(4 + 2) + (7 + 2)



9. a) What is cascading problem in dynamic CMOS logic ?
How is this problem removed ?

- b) Design the following function using Domino logic :

$$F1 = A' + BCD + D'$$

$$F2 = DE + (A + C'G + HF1)'$$

$$F3 = (IJK' + (F1'F2)') + AB'C \quad (3 + 3) + 9$$

10. a) Draw the layout for 2bit full adder.

- b) Describe read and write operations of a DRAM cell.

$$9 + (3 + 3)$$

11. a) Design the ROBDD of 4 bit full adder.

- b) Explain with illustrations Moore's and Mealy machines.

$$9 + (3 + 3)$$

=====