 



.....
Head-Examiner/Co-Ordinator/Scrutineer



DO NOT WRITE ON THIS PAGE



 CS/M.TECH (ECE)/SEM-2/EC-1002/09
ADVANCED ANALOG INTEGRATED CIRCUIT DESIGN
SEMESTER - 2



Time : 3 Hours]

Full Marks : 70

The figures in the margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

GROUP - A

Answer Question No. 1 and any *two* from the rest.

1. Write short notes on any *three* of the following : 3 × 5 = 15
 - i) Critical field in DSM Technology
 - ii) Logical effort
 - iii) Elmore Delay
 - iv) Stray insensitive switching capacitor realization of a non-inverting integrator
 - v) Sizing an inverter.

2. What is meant by velocity saturation in short channel MOS gates and how it affects the pinch-off point, $V_{D, sat}$? Determine the value of $V_{D, sat}$ for an NMOS device assuming $V_{GS} = 1.8$ V, $V_T = 0.5$ V and Channel length = 180 nm.

(Given, critical electric field for electrons, $E_{cn} = 6 \times 10^4$ V/cm) 2 + 4 + 4

3. Design a suitable circuit to implement an 8-input AND gate to drive a capacitor load of 200 fF and with an input capacitance limited to 10 fF with the smallest delay. Justify your steps. 10



4. What is interconnect in VLSI and how it has become so important now ? Show the variation of gate delay and interconnect delay with minimum feature size.



A uniform polysilicon interconnect of length 0.5 mm and width 5 μm is used at a gate output. Estimate the total delay using a lumped RC. 10

Assume : [i) sheet resistance $30\Omega/\square$

ii) unit area capacitance = $0.066 \text{ fF}/\mu\text{m}^2$

iii) unit length capacitance = $0.046 \text{ fF}/\mu\text{m}$]

5. Explain clearly how a switched capacitor can be used to replace a resistance in integrated circuits. Mention its advantages and disadvantages. Design a switched capacitor filter using a high gain Op-Amp with the following frequency response :

- i) gain 20 db from 0 to 1 kHz.
ii) gain drops uniformly at 20 db/decade after 1 kHz and becomes 0 db at 10 kHz.

Use a clock of $2\pi \times 100 \text{ kHz}$ and assume the value of the switched capacitor between output and op-amp input terminal = 100 fF. 3 + 2 + 5

GROUP - B

Answer Question No. 6 & any two from the rest.

6. Why in case of a single ended differential amplifier one I/P terminal is marked as (-) and another one as (+ ve) ? 5
7. What is the block diagram of a CMOS Op-Amp ? Design any 2 stage CMOS Op-Amp. 5 + 10
8. Design cascode current sink circuit and mention its advantages.
If $\Delta k' / k' = \pm 5\%$ & $\Delta V_T / (V_{GS} - V_T) = \pm 10\%$, then what will be the error in current mirror gain ? 8 + 3 + 4



9. Explain with a circuit diagram, the operation of a differential amplifier. What is CMRR ? Determine the CMRR of the foll. circuit.

10 + 5



Dia.

10. Define current source & sink. Show how the O/P resistance of a current sink can be increased.

Explain the operation of a band gap voltage reference source in a VLSI circuit.

5 + 7 + 3

END