



Name :
Roll No. :
Invigilator's Signature :

CS/M.TECH (EE)/SEM-2/PSM-204(A)/2011

2011

HIGH VOLTAGE DC TRANSMISSION

Time Allotted : 3 Hours

Full Marks : 70


The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

Answer any *five* questions.

$5 \times 14 = 70$

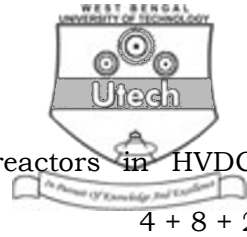1. A three phase, 12 pulse rectifier is fed from a transformer with nominal voltage ratings of 220KV/110KV.
 - a) If the primary voltage is 230 KV and the effective turns ratio T is 0.48, determine the dc output voltage when the ignition delay angle α is 20° and the commutation angle μ is 18° .
 - b) If the direct current delivered by the rectifier is 2000A, calculate the effective commutating reactance X_c , RMS fundamental component of alternating current, power factor $\cos \phi$, and reactive power at the primary side of the transformer. Draw the HVDC system.



- c) Write the purpose of smoothing reactors in HVDC system. 4 + 8 + 2
2. a) Discuss the causes and consequences of commutation failure in inverters with proper diagrams.
- b) Explain the requirements and sources of reactive power in converters. 10 + 4
3. For a 3ϕ , 6 pulse, full wave, full controlled converter bridge explain the operation of the converter. Hence with necessary circuit diagram and graphs deduce the following.
- a) Average no-load direct voltage with & without ignition delay ' α '.
- b) RMS value of the fundamental frequency component of the alternating line current.
- c) Currents of an outgoing and an incoming valve respectively during commutation. 4 + 4 + 2 + 4
4. a) In a 6 pulse full wave bridge converter with ignition angle α and overlap angle μ , find the voltage drop due to overlap. Hence derive the expression of equivalent commutating resistance. Draw necessary wave forms.



- b) Calculate the necessary secondary line voltage of the transformer for a 3ϕ bridge rectifier to provide a voltage of 110 KV. Assume $\alpha = 25^\circ$, $\mu = 12^\circ$. Calculate the effective reactance X_c if the rectifier is delivering a current $I_d = 750$ A. 4 + 2 + 2 + 6
5. a) Discuss the basic principles of DC link control.
- b) Describe in details the different control characteristics. Draw the basic control scheme. 3 + 8 + 3
6. a) State the advantage and disadvantage of 12 pulse converter over 6 pulse.
- b) Deduce the total harmonic analysis of a 12 pulse converter. 4 + 10
7. Discuss Mode 1, Mode 2, Mode 3 operations of a 2 terminal HVDC system with necessary equations and diagram. 14
-