

Name : .....  
Roll No. : .....  
Invigilator's Signature : .....

**CS / M.TECH (VLSI) / SEM-1 / MVLSI-103 / 2010-11**

**2010-11**

**ADVANCED DIGITAL INTEGRATED CIRCUIT DESIGN**

Time Allotted : 3 Hours

Full Marks : 70

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable.*

*Answer Q.No.1 and any four from the rest.*

**GROUP – A**

**( Short Answer Type Questions )**

1. Answer any *seven* questions : 7 × 2
- i) What is 'keeper ckt' ? Draw and explain.
  - ii) Differentiate between software simulators and hardware emulators.
  - iii) What is meant by the strength of a gate ? Give an example of a weak gate.
  - iv) What is critical path ?
  - v) State the steps in a synthesis procedure.
  - vi) What is the function of an Arbiter ?



- vii) State the differences between high-level synthesis, logic synthesis and physical synthesis.
- viii) What was the motivation for using asynchronous circuits ?
- ix) Define the term 'O(n<sup>2</sup>) time complexity'.
- x) What are the inputs and outputs of the placement procedure ?

**GROUP - B**


**( Long Answer Type Questions )**

Answer any *four* of the following.  $4 \times 14 = 56$


- 2. a) Explore the different factors limiting the size reduction of CMOS devices.
- b) What is 'one-hot encoding' ? Clarify the advantages and disadvantages.  $7 + 3 + 4$
- 3. a) What is clock skew ? How is it controlled ?
- b) Explain qualitatively the 'genetic algorithm' as applicable to placement.
- c) What types of design information do the following formats carry?  $5 + 6 + 3$   
SDF, EDIF, GDSII
- 4. a) What is the problem with domino logic ?
- b) Clarify with Generic structure of NORA logic circuit how the problem is overcome.
- c) What is 'hardware accelerated simulation' ?  $4 + 7 + 3$



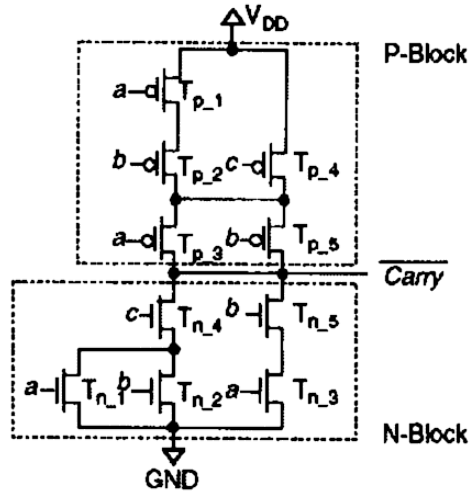5. a) Optimize the circuit for equal rise and fall times :



 - b) Draw and explain a CAM-structure with its operation and application. 5 + 9
6. a) What are the various sources of parasitic capacitances, inductances and resistances in a VLSI circuit ?
- b) Draw and explain the two-phase routing flow.
- c) Calculate the logical efforts of the gates shown :



5 + 5 + 4

7. a) What are the various timings associated with a circuit performance ? Explain.



- b) Draw the binary tree of the following Boolean equation and reduce it to ROBDD.

$$f = \bar{x}_1x_2x_3 + x_1\bar{x}_2x_3 + x_1x_2$$

- c) What are the advantages and disadvantages of TG ?  
Design a mux using TG. 5 + 3 + 3 + 3

8. a) What are the different types of scaling ? Compare them.
- b) Implement an order in a PGCA.
- c) Construct a stick diagram of a single-bit full-adder by first drawing its transistor schematic. 6 + 3 + 5

=====