



Name :

Roll No. :

Invigilator's Signature :

CS/M.TECH(ECE-VLSI)/SEM-2/MVLSI-203/2013

2013

ANALOG IC DESIGN

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

Answer Q. No. **1** and any *four* from the rest. $5 \times 14 = 70$

GROUP – A

1. Answer the following questions :

- a) What are the advantages of MOSFET resistor ? 3
- b) Explain the characteristics of an ideal current sink. 2
- c) Describe how a MOSFET can work as a Diode. 2
- d) Explain how a combination of switches and capacitors
can be used to emulate a resistor. 3
- e) Describe the velocity saturation and channel length
modulation in a n -MOS structure. 2
- f) What is a Phase Locked Loop ? Mention two uses of it. 2

GROUP – B




Answer any *four* questions.

4 × 14 = 56

2. Explain the basic operation of a two-stage Open loop Comparator. Design an Integrator circuit using Switched capacitor configuration and describe its operation. 7 + 7
3. Explain the operation of a Differential amplifier with a current mirror load. How can a MOS device be used as a Voltage reference ? Explain the operation of a Band-Gap voltage reference source in a VLSI circuit. 5 + 4 + 5
4. Draw the circuit diagram of dual slope A/D converter and explain its operation. Discuss the merits and demerits of Flash ADC. Find the resolution for a DAC, if the output voltage is desired to be changed by 1 mV step-size with a reference voltage of 5 V. 7 + 3 + 4
5. Write a short note on how MOSFET can work as current sink and source. How to improve the performance of a simple NMOS current sink by connecting a resistance between source and ground ? 6 + 8



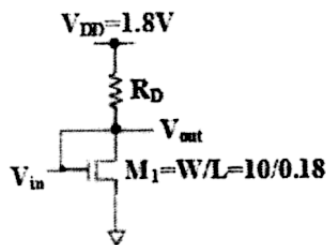6. Design and explain the MOSFET switch model. Why subthreshold region operation has become very popular for analog VLSI circuits ? Explain the importance of g_m / I_d and intrinsic gain in sub-micron analog circuits. 3 + 3 + 8
7. Design a small signal equivalent circuit of a MOSFET. Explain how MOSFET can be used as a diode and compare it with a conventional $P-N$ junction diode. Calculate the small signal voltage gain of CS stage shown in the figure below, $I_D = 1\text{mA}$, $\mu_n C_{ox} = 100\text{ }\mu\text{A/V}^2$, $V_{th} = 0.5\text{V}$ and $\lambda = 0$. Verify that M_1 operates in saturation.



3 + 5 + 6

=====