

Name :

Roll No. :

Invigilator's Signature :

CS / M.TECH(ECE-VLSI) / SEM-2 / MVLSI-203 / 2012

2012

ANALOG IC DESIGN

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

Answer Question No. 1 and any four from the rest.

1. a) In Fig. 1, calculate the minimum output voltage required to keep the device in saturation. 2


 


Fig.1

 - b) How threshold voltage of MOSFET shifts due to body bias effect ? 2
- c) How NMOS transistor can be used as linear resistor ? 2



- d) For CMOS push-pull inverter shown in Fig.2, find the small signal voltage gain A_v if $I_D = 200\mu A$, $\frac{W_1}{L_1} = \frac{W_2}{L_2} = \frac{5\mu m}{1\mu m}$, $C_{gd1} = C_{gd2} = 5fF$, $C_{bd1} = C_{bd2} = 30fF$ and $C_L = 10PF$. 2

 


Fig.2

- e) What is clock feed-through? 2
 f) Explain one advantage and one disadvantage of depletion type NMOS over enhancement type NMOS device. 2
 g) Calculate the intrinsic gain of an NMOS device operating in saturation with $\frac{W}{L} = \frac{50}{0.5}$ and $|I_D| = 0.5\text{ mA}$. 2
2. Explain common source single stage amplifier with source degeneration. How does common gate stage differ from common source stage? Derive and calculate the voltage gain of a common gate stage with a current source load as shown in Fig. 3. Explain the circuit operation of folded cascade stage.

4 + 2 + 4 + 4


 


Fig . 3

 

3. a) What is differential pair ? Derive and explain quantitative analysis of basic differential pair circuit.

2 + 6

- b) A differential pair uses input NMOS devices with $\frac{W}{L} = \frac{50}{0.5}$ and tail current of 1mA.

(i) What is the equilibrium overdrive voltage of each transistor ?

(ii) How is the tail current shared between the two sides if $V_{in_1} = V_{in_2} = 50\text{mV}$? 3 + 3

4. Explain basic concepts and performance parameters of CMOS operational amplifier. Explain the MOS two-stage operational amplifier in detail. What are the various referenced biasing techniques used in the MOSFET ?


4 + 6 + 4

5. What is DAC ? Explain $\frac{D}{A}$ conversion principle in detail.

What are the basic parameters and terminologies associated with the performance of practical $\frac{D}{A}$ converter circuits ?

Explain flash type ADC. 1 + 6 + 4 + 3

 6. What do you understand by "switched capacitor" ? Explain basic switched capacitor operation in detail. Give detail explanation about switched capacitor integrator. 2 + 6 + 6



7. Derive and explain fundamental concept of N-channel current mirror. What are the applications of ideal current and voltage references in analog circuit design ? Fig. 4 illustrates a reference circuit that provides a reference voltage output. Derive a symbolic expression of V_{ref} . Draw and explain Wilson-current mirror. What are the basic differences between Wilson-current mirror and cascade current mirror ?

3 + 2 + 3 + 4 + 2

 


Fig. 4

8. What do you understand by PLL ? Explain the principle of operation of PLL system. Explain capture phenomenon and tracking characteristics of PLL in detail. Explain the operation of VCO with neat diagram.

2 + 4 + 5 + 3