

Name : .....

Roll No. : .....

Invigilator's Signature : .....

**CS / B.TECH (ECE) / SEM-4 / EC-402 / 2011**

**2011**

### **DIGITAL ELECTRONIC CIRCUITS**

Time Allotted : 3 Hours

Full Marks : 70

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words  
as far as practicable.*

#### **GROUP – A**

##### **( Multiple Choice Type Questions )**

1. Choose the correct alternatives for any ten of the following :

$$10 \times 1 = 10$$

- i) The Excess-3 representation of decimal 59 is
- a) 01100010                          b) 00111110
- c) 10001100                          d) none of these.
- ii) The number of full address required to construct an  $m$ -bit parallel adder is
- a)  $m/2$                                   b)  $m - 2$
- c)  $m$     d)  $m + 1$ .

CS / B.TECH (ECE) / SEM-4 / EC-402 / 2011

iii) The 2's complement representation of  $(-19)_{10}$  is

- a) 101100
- b) 101110
- c) 101101
- d) none of these.

iv) The maxterm corresponding to decimal 9 is

- a)  $A B' C' D$
- b)  $A + B' + C' + D$
- c)  $A' + B + C + D'$
- d)  $A' B C D'$ .

v) The number of comparators required in a 8-bit flash type A/D converter is

- a) 256
- b) 255
- c) 64
- d) 8.

vi) A 3-bit synchronous counter uses flip-flops with propagation delay of 20 ns each. The maximum possible time required for change of state will be

- a) 60 ns
- b) 40 ns
- c) 20 ns
- d) none of these.



CS / B.TECH (ECE) / SEM-4 / EC 402 / 2011

vii) The number of EX-OR gates required for the conversion of 11011 to its equivalent Gray code is

- a) 2
- b) 3
- c) 5
- d) 4.

viii) A mod-2 counter followed by a mod-5 counter is

- a) same as a mod-5 counter followed by a mod-2 counter
- b) a decade counter
- c) a mod-7 counter
- d) none of these.

ix) Which family has better noise margin ?

- a) ECL
- b) DTL
- c) TTL
- d) MOS.

x) The number of  $D$  flip-flops required to design a mod-10 ring counter is

- a) 5
- b) 10
- c) 9
- d) 8.

CS / B.TECH (ECE) / SEM-4 / EC-402 / 2011






**GROUP – B**

**( Short Answer Type Questions )**

Answer any *three* of the following.  $3 \times 5 = 15$

2. Design a Full Adder circuit using a decoder and other necessary logic gates. Assume that the decoder has all active low outputs. 5
  3. Design a S-R flip-flop with the help of J-K flip-flop. 5
  4. Implement a 16:1 MUX by using 4 : 1 MUX only. 5




CS / B.TECH (ECE) / SEM-4 / EC 402 / 2011

5. a) Distinguish between synchronous and Asynchronous counters. 2
- b) Calculate the frequency of 4-bit ripple counter, if the period of waveform at the last flip-flop is 64 microsecond. 3
6. Design a Binary to Gray code converter using PROM. 5

**GROUP – C****( Long Answer Type Questions )**Answer any *three* of the following.  $3 \times 15 = 45$ 

 7. a) Design a sequential circuit that implements the following state diagram. (Use *D* flip-flop) 10



- b) Implement the following Boolean function using 8 : 1 MUX :

$$F(A, B, C, D) = \sum m(0, 7, 8, 9, 10, 11, 15). \quad 5$$

CS / B.TECH (ECE) / SEM-4 / EC-402 / 2011



8. a) Design a MOD-6 synchronous up-counter using J-K flip-flops. 7

- b) Implement the following function using  $3 \times 4 \times 2$  PLA :

$$F_1(A, B, C) = \sum m(3, 5, 6, 7) \quad F_2(A, B, C) = \sum (0, 2, 4, 7). \quad 8$$

9. a) Simplify the following function in SOP form using Quine MC-Cluskey method :

$$F(A, B, C, D) = \sum m(0, 1, 4, 7, 9, 11, 13, 15) + \sum d(3, 5). \quad 9$$

- b) Describe the operation of a two-input NAND gate constructed with CMOS. 6

10. a) Design a combinational circuit for Excess-3 code to BCD conversion using minimum number of logic gates.

9

- b) Describe the principle of operation of successive Approximation type A/D converter. 6

4053

6

CS / B.TECH (ECE) / SEM-4 / EC 402 / 2011



3 × 5

11. Write short notes on any *three* of the following :

- a) 4-bit magnitude comparator
- b) Bi-directional shift register
- c) PAL
- d) Master-slave J-K flip-flop
- e) EEPROM.

=====