



ENGINEERING & MANAGEMENT EXAMINATIONS, JUNE - 2009
DIGITAL ELECTRONIC CIRCUITS
SEMESTER - 4

Time : 3 Hours]

[Full Marks : 70

GROUP - A**(Multiple Choice Type Questions)**

1. Choose the correct alternatives for any ten of the following : $10 \times 1 = 10$

i) Gray code of 1011 (binary) =

a) 0101

b) 1101

c) 1110

d) none of these.

ii) An example of reflected code is

a) BCD

b) ASCII

c) GRAY

d) Hamming code. iii) If $(212)_x = (23)_{10}$ where x is base (+ ve integer) then the value of x is

a) 2

b) 3

c) 4

d) 5. iv) Excess-3 code 3d representation of $(19)_{10}$ is

a) 10011

b) 00011001

c) 01001100

d) 11000100. v) The decimal equivalent of the binary number $(101111.1101)_2$ isa) $(46.8125)_{10}$ b) $(47.8125)_{10}$ c) $(47.8155)_{10}$ d) $(47.8145)_{10}$.



vi) A 10 MHz signal is applied to a MOD 5 counter followed by a MOD 8 counter.

The output frequency will be

- | | |
|-----------|------------|
| a) 10 kHz | b) 2.5 kHz |
| c) 5 kHz | d) 25 kHz. |

vii) A 4-stage ripple counter counts up to

- | | |
|-------|-------|
| a) 12 | b) 15 |
| c) 11 | d) 4. |

viii) Which family has the better noise margin ?

- | | |
|--------|---------|
| a) ECL | b) MOS |
| c) DTL | d) TTL. |

ix) A 4-variable logic expression can be realized by using only one

- | | |
|-----------------------|------------------------|
| a) 4-input NOR gate | b) 4 : 1 demultiplexer |
| c) 16 : 1 multiplexer | d) none of these. |

x) D flip-flop can be used as a

- | | |
|--------------------|-------------------|
| a) divider circuit | b) delay switch |
| c) differentiator | d) none of these. |

xi) Master-slave configuration is used in flip-flops to

- | |
|------------------------------------|
| a) increase its clocking rate |
| b) reduce power dissipation |
| c) eliminate race around condition |
| d) improve its reliability. |



xii) The output frequency of a decade counter clocked from a 50 kHz signal is

- | | |
|-----------|------------|
| a) 50 kHz | b) 500 kHz |
| c) 5 kHz | d) 25 kHz. |

xiii) The number of D flip-flops required to design a mod-10 Ring counter is

- | | |
|------|-------|
| a) 5 | b) 10 |
| c) 9 | d) 8. |

xiv) The power consumption of the dynamic RAM is

- | | |
|---------------------------------|---------------------------------|
| a) equal to that of static RAM | b) more than that of static RAM |
| c) less than that of static RAM | d) almost zero. |

xv) The hexadecimal equivalent number of (7324.456)₈ is

- | | |
|------------|-------------|
| a) ED 4.87 | b) ED 4.47 |
| c) ED 4.57 | d) ED 4.97. |

GROUP - B

(Short Answer Type Questions)

Answer any three of the following questions.

$3 \times 5 = 15$

2. Design a logic diagram, using logic gates, for addition / subtraction circuit, using a control variable P such that this operates as full adder when $P = 0$, and full subtractor for $P = 1$.
3. Design a J-K F/F using a D F/F, a 2 : 1 MUX and one inverter.
4. Design a 2-input NAND gate using MOS inverter.
5. Implement the following function using 4 : 1 MUX only :

$$F = \sum m (0, 2, 3, 6, 8, 9, 12, 14)$$

6. Implement the full-adder circuit using a 3 to 8 decoder with all active low output and additional logic gates, if required.

4463 (08/08)

**GROUP - C****(Long Answer Type Questions)**Answer any *three* of the following questions. $3 \times 15 = 45$

7. a) Draw and explain the circuit of BCD adder using commercially available adder IC 7483 and other necessary logic gates. 7

- b) Simplify the following using Quine McClusky method :

$$F(W, X, Y, Z) = \sum(0, 1, 2, 5, 8, 14) + \sum d(4, 10, 13).$$

8

8. a) What is CLA adder ? Define the terms 'carry propagate' and 'carry generate'. The propagation delay of EX-OR gate is 20ns and that of OR and AND gate is 10ns. Find the propagation delay of a CLA adder. $2 + 3 + 2$

- b) "Excess-3 code is self-complementing." Explain the statement and write its application. 4

- c) Implement the following function using a $3 \times 4 \times 2$ PLA :

$$F_1(A, B, C) = \sum(3, 5, 6, 7)$$

$$F_2(A, B, C) = \sum(0, 2, 4, 7).$$

4


9. a) With the help of necessary circuit diagram, explain the operation of dual slope ADC. 9

- b) A 4-bit binary ladder D/A converter with $R = 10 \text{ k}\Omega$ uses a reference of 5 V. Find the following :

- i) Ideal scale factor in V/step
- ii) Analog output corresponding to the binary input 0110
- iii) Resolution in %
- iv) Full scale output
- v) Maximum deviation in volts from the best straight line in order to meet standard linearity. 6



 10. a) Design a sequential circuit that implement the following state diagram. Use all D-type F/F for the design. 9



- b) Draw and explain the 4 bit bi-directional Shift Register using mode control (M), when M is logic zero then left shift an right shift for M is logic one. 6

11. Write short notes on any three of the following : 3 x 5

- a) D.C. noise margin and A.C. noise margin
- b) Hold time and set-up time related to FF
- c) Parity generator and checker
- d) Tri-state gates in TTL family
- e) EPROM.

END