	Utech
Name :	
Roll No.:	To Dynamic (y Saming and Saphan)
Invigilator's Signature :	•••••

ELECTRICAL & ELECTRONICS MEASUREMENT

Time Allotted: 3 Hours Full Marks: 70

The figures in the margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

GROUP – A (Multiple Choice Type Questions)


1. Choose the correct alternatives for any ten of the following:

 $10 \propto 1 = 10$

- i) A Wheatstone bridge cannot be used for precission measurements because errors due to
 - a) resistance of connecting leads
 - b) thermo-electric emf
 - c) contact resistance
 - d) all of these.
- ii) Maxwell's inductance-capacitance bridge is
 - a) Low Q coils
 - b) Medium Q coils
 - c) High Q coils
 - d) Low and Medium Q coils.

44005 [Turn over

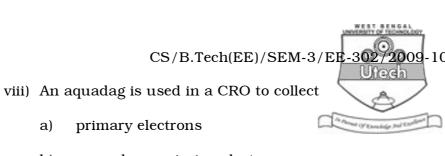- iii) Electrodynamic type instruments can be used as
 - a) standard instruments only
 - b) transfer instruments only
 - c) both standard and transfer instruments
 - d) indicator type instruments.
- iv) Megger is used for the measurement of
 - a) low resistance
- b) medium resistance
- c) high resistance
- d) none of these.
- v) The time base of a CRO is developed by
 - a) squared waveform
- b) saw-tooth waveform
- c) sine waveform
- d) none of these.
- vi) In an electrodynamic type watmeter
 - a) the current coil is made fixed
 - b) the pressure coil is made fixed
 - c) any of the current or pressure coil can be made fixed
 - d) both coils are movable.
- vii) In a CRT, the focusing anode is located
 - a) between pre-acelarating and acelarating anode
 - b) after acelarating anode
 - c) before pre-acelarating anode
 - d) none of these.



- secondary emission electrons b)
- both primary and secondary emission electrons c)
- none of these. d)
- ix) LVDT is a

a)

- a) capasitive transducer
- b) resistive transducer
- c) inductive transducer
- none of these. d)
- Which of the following devices cannot be used to X) measure pressure?
 - Strain gauge a)
- b) LVDT
- Piezoelectric crystal c)
- Pyrometer. d)
- The torque/weight ratio of a Dynamometer instrument xi) is
 - a) small


- b) high
- medium c)
- d) none of these.

44005


3

[Turn over



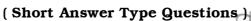


Answer any three of the following.

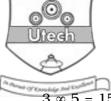

- 2. Show that the driving torque in a moving iron instrument is given by $T_d = \frac{1}{2} i^2 \frac{dL}{dQ}$ where symbols have thier usual meaning.
- 3. What difficulties are encountered in measuring high resistance? What is a guard circuit?
- 4. What are the absolute and secondary instruments? What are the advantages of electronic instruments?
- 5. Explain the procedure of measurement of high voltage by d.c. potentiometer.
- 6. How can you measure the phase difference between two sinusoidal signals using a CRO ?

44005

4

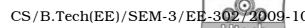

GROUP - C

(Long Answer Type Questions)

Answer any three of the following.

7. Develop the torque equation of Moving Coil Instrument. a)

8

- A moving coil ammeter has a fixed shunt of 0.02Ω with b) a coil resistance of $R = 1000 \Omega$ and a potential difference of 500 mV across it. Full scale deflection is obtained.
 - To what shunted current does it corresponds? i)
 - Calculate the value of R to give full scale deflection ii) when shunted current I is
 - 20 amp
 - 60 amp
 - With what value of R is 45% deflection obtained with I = 100 A? 5
- Draw the circuit diagram of an Electrodynamic c) wattmeter with power lebelling.
- 8. Draw the diagram of laboratory type (Cormpton's) D.C. a) potentiometer. What is meant by standardization of potentiometer? 6
 - b) How can a potentiometer be used
 - for calibration of a voltmeter i)
 - ii) for calibration of a wattmeter?


6

Voltage drop across the low resistance under test is c) 0.83942 V. Voltage drop across a standard resistance connected in series with the unknown is 1.01575. If the value of standard resistance is 1.0014Ω . Calculate the value of unknown resistance. 3

- 9. a) What are the advantages and disadvantages of electrodynamometer type instruments?
 - b) A simple shunted ammeter using a basic meter movement with an internal resistance of $1800~\Omega$ and a full scale deflection current of $100~\mu A$ is connected in a circuit and gives reading of 3.5~mA on its 5~mA scale. The reading is checked with a recently calibrated d.c. ammeter which gives a reading of 4.1~mA. The implication is that the ammeter has a faulty shunt on its 5~mA range. Calculate
 - i) the actual value of faulty shunt
 - ii) the current shunt for the 5 mA range.

7

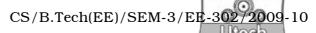- 10. a) Draw the equivalent circuit and phasor diagram of a current transformer.
 - b) Derive the expression for the ratio and phase angle errors.
- c) Explain the difference between CT and PT. 4 + 8 + 344005 6



- 11. a) Draw the block diagram of a CRO and explain different of the function of the different blocks.
 - b) What are the function of Time-base generator in CRO?

3

c) What are Lissajous figures ? Explain how phase and frequency can be measured using these figures. 1+3

44005 7 [Turn over