

CS/B.Tech/EE/EEE/ICE/Odd/Sem-3rd/EC(EE)-302/2015-16



**MAULANA ABUL KALAM AZAD UNIVERSITY OF TECHNOLOGY,
WEST BENGAL**

EC(EE)-302

DIGITAL ELECTRONIC CIRCUIT

Time Allotted: 3 Hours

Full Marks: 70

*The questions are of equal value.
The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable
All symbols are of usual significance.*

**GROUP A
(Multiple Choice Type Questions)**

1. Answer any *ten* questions. 10×1 = 10
- (i) The number of bit required to represent an eight digit decimal number in BCD is
 (A) 8 (B) 16
 (C) 24 (D) 32
- (ii) All Boolean expression can be implemented with
 (A) NAND gate only (B) NOR gate only
 (C) Combination of all basic gates (D) Any of these
- (iii) The minimum number of NAND gates required to implement the Boolean function $A + \bar{A}B + A\bar{B}C$ is
 (A) three (B) two
 (C) one (D) zero

3105

1

Turn Over

CS/B.Tech/EE/EEE/ICE/Odd/Sem-3rd/EC(EE)-302/2015-16

- (iv) Which of the following flip-flop is used as a latch?
 (A) J-K flip-flop (B) S-R flip-flop
 (C) D flip-flop (D) T flip-flop
- (v) A full adder can be made out of
 (A) two half adder (B) two half adder and an inverter
 (C) two half adder and a OR gate (D) two half adder and a AND gate
- (vi) An asynchronous counter is also known as
 (A) ripple counter (B) multiple clock counter
 (C) decade counter (D) modulus counter
- (vii) A MOD 13 counter must have
 (A) 13 flip-flop (B) 3 flip-flop
 (C) 4 flip-flop (D) 2 flip-flop
- (viii) Which of the following is an invalid state of an 8241 BCD counter?
 (A) 0010 (B) 0101
 (C) 1000 (D) 1100
- (ix) The fan out of a logic gate refers to number of
 (A) input device that can be connected
 (B) input terminal
 (C) output terminal
 (D) circuit that can be connected at the output
- (x) Static RAM is preferred over dynamic RAM when the requirement is of
 (A) slow speed of operation (B) large storage capacity
 (C) lower access time (D) lower power consumption
- (xi) A PLA can be used
 (A) as a microprocessor (B) as a dynamic memory
 (C) to realize a sequential circuit (D) to realize a combinational circuit

3105

2

C/S/B.Tech/EE/EEE/ICE/Odd/Sem-3rd/EC(EE)-302/2015-16

C/S/B.Tech/EE/EEE/ICE/Odd/Sem-3rd/EC(EE)-302/2015-16

GROUP B
(Short Answer Type Questions)

Answer any *three* questions.

3 × 5 = 15

2. Obtain the logic expression for a 3-input majority function and hence implement it using only NAND gates.
3. Design 4:1 multiplexer using 2:1 multiplexer.
4. Prove that $(A + B)(\bar{A} + C)(B + C) = (A + B)(\bar{A} + C)$.
5. Using 2's complement method subtract $(101101)_2$ from $(1011101)_2$.
6. Convert J-K flip-flop to D flip-flop.

GROUP C
(Long Answer Type Questions)

Answer any *three* questions.

3 × 15 = 45

7. (a) Simplify the following function using K-map:

$$f = \sum m(0, 5, 8, 10, 11, 14, 15) + \sum d(3, 13).$$

(b) What are the difference between minterms and maxterms?

(c) Prove Distributive law and Absorption law.
8. (a) What is the difference between full-adder and full-subtractor?
- (b) Show how a full-adder can be converted to a full-subtractor with the addition of an inverter circuit.

- (c) Design a full subtractor using two half-subtractors and one extra gate, if necessary.

9. (a) Describe the operation of successive approximation type ADC.
- (b) Explain the sequence of operation of conversion of an analogue signal to its digital equivalent when the expected digital output is 1010.
- (c) Define quantizing error for an ADC.

10. (a) What is the significance of the logic family with reference to digital Integrated Circuits (ICs)?

- (b) What is the totem-pole output stage? What are its advantages?

- (c) Implement the following functions using PROM:

$$F1(A, B, C) = \sum m(0, 2)$$

and

$$F2(A, B, C) = \sum m(1, 4, 7)$$

11. Write short notes on any *three* of the following:

- (a) Lock-out phenomena in counters
- (b) Irregular counter
- (c) PAL
- (d) Encoder
- (e) CMOS and its operation