

CS/B.Tech/EE/EVEN/SEM-6/EE-603/2015-16

CS/B.Tech/EE/EVEN/SEM-6/EE-603/2015-16



**MAULANA ABUL KALAM AZAD UNIVERSITY OF
TECHNOLOGY, WEST BENGAL**
Paper Code : EE-603
POWER ELECTRONIS

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own
words as far as practicable.*

GROUP - A
(Multiple Choice Type Questions)

1. Choose the correct alternatives for any *ten* of the
following : $10 \times 1 = 10$

- i) An IGBT has three terminals called
- a) collector, emitter and base
 - b) drain, source and base
 - c) drain, source and gate
 - d) collector, emitter and gate.

- ii) In an SCR
- a) latching current $L I$ is associated with turn-off process and holding current $H I$ with turn-on process
 - b) both $L I$ and $H I$ are associated with turn-off process
 - c) $H I$ is associated with turn-off process and $L I$ with turn-on process
 - d) both $L I$ and $H I$ are associated with turn-on process.
- iii) For an SCR, (dv/dt) protection is achieved through the use of
- a) RL in series with SCR
 - b) RC across SCR
 - c) L in series with SCR
 - d) RC in series with SCR.
- iv) In a CSI, if frequency of output voltage is f Hz, then frequency of voltage input to CSI is
- a) f b) $2f$
 - c) $f/2$ d) $3f$.

CS/B.Tech/EE/EVEN/SEM-6/EE-603/2015-16

- v) The reverse recovery characteristics of a power diode is due to
 - a) stored charge in depletion layer
 - b) stored charge in semiconductor layers
 - c) stored charge in both depletion and semiconductor layers
 - d) none of these.
- vi) HVDC transmission is preferred to EHV-AC transmission because
 - a) HVDC terminal equipment are expensive
 - b) VAR compensation is not required for HVDC systems
 - c) system stability can be improved
 - d) harmonic problem is avoided.
- vii) A freewheeling diode is placed across the *dc* load
 - a) to prevent reversal of load voltage
 - b) to permit transfer of load current away from the source
 - c) both (a) and (b)
 - d) none of these.

CS/B.Tech/EE/EVEN/SEM-6/EE-603/2015-16

- viii) The features of chopper drives are
 - a) smooth control but slow response
 - b) smooth control but fast response
 - c) fast response with smooth control but less efficient
 - d) none of these.
- ix) In *dc* chopper, the load voltage is governed by
 - a) number of thyristors used in the circuit
 - b) duty cycle of the circuit
 - c) *dc* voltage applied to circuit
 - d) none of these.
- x) In resonant pulse inverters
 - a) *dc* output voltage variation is wide
 - b) the frequency is low
 - c) output voltage is never sinusoidal
 - d) *dc* saturation of transformer core is minimized.
- xi) Cycloconverter converts
 - a) *ac* voltage to *dc* voltage
 - b) *dc* voltage to *dc* voltage
 - c) *ac* voltage to *ac* voltage at same frequency
 - d) *ac* voltage at supply frequency to *ac* voltage at load frequency.

xii) The metal oxide varistor (MOV) is used for protecting

- a) gate circuit against over currents
- b) gate circuit against overvoltages
- c) both (a) and (b)
- d) none of these.

GROUP – B

(Short Answer Type Questions)

Answer any *three* of the following. $3 \times 5 = 15$

2. Describe the different modes of operation using static $V-I$ characteristics of thyristor. What is the effect of gate current on the characteristics ?
3. Draw and explain circuit diagram for the synchronized UJT triggering. Also draw the associated voltage waveforms.
4. Discuss a comparison between power transistors, power MOSFET & IGBT in relation to their application in power electronics.
5. How the power factor of a single phase half-wave converter can be improved using freewheeling diode ? Explain with proper circuit diagram and waveforms.
6. Describe the effect of source inductance on the DC output voltage of a single phase full controlled bridge converter.

GROUP – C

(Long Answer Type Questions)

Answer any *three* of the following. $3 \times 15 = 45$

7. a) Describe the different modes of operation using static $V-I$ characteristics of Thyristor. What is the effect of gate current on this characteristics ? $5 + 2$
- b) How di/dt and dv/dt protections are achieved in SRC ? $4 + 4$
8. a) A single-phase fully controlled bridge converter supplies an inductive load. Assuming that the output current is virtually constant and is equal to I_d . Determine the following performance measures if the supply voltage is 230V and if the firing angle is maintained at $\pi/6$ radians.
 - i) Average output voltage
 - ii) Supply RMS current
 - iii) Supply fundamental RMS current
 - iv) Fundamental power factor
 - v) Supply power factor
 - vi) Supply harmonic factor
 - vii) Voltage ripple factor. 8
- b) What is the difference between semi-converter and full-converter ? Why semi-converter is single quadrant whereas full-converter is two quadrant converters ? $3 + 4$

CS/B.Tech/EE/EVEN/SEM-6/EE-603/2015-16

9. a) What is the principle of operation of boost regulator ? 5
- b) A *dc* battery is charged from a constant *dc* source 220 V through a chopper. The *dc* battery is to be charged from its internal *emf* of 90 V to 122 V. The battery has internal resistance of 1Ω . For a constant charging current of 10A, calculate the range of duty cycle. 5
- c) Explain briefly the working of class C chopper with relevant diagrams. 5
10. a) Explain the basic principle of step up and step down cyclo-converter. 4 + 4
- b) For a single phase *ac* voltage regulator feeding a resistive load, draw the waveforms of source voltage, gating signals, output voltage, source and output currents and voltage across SCRs. 7
11. Write short notes on any *three* of the following : 3 × 5
 - a) Series operation of SCRs
 - b) Chopper controlled *dc* motor
 - c) UPS
 - d) Powerdiodes
 - e) TRIAC.