

CS/B.TECH/EE/EVEN/SEM-6/EE-603/2018-19



**MAULANA ABUL KALAM AZAD UNIVERSITY OF
TECHNOLOGY, WEST BENGAL**

Paper Code : EE-603

POWER ELECTRONICS

Time Allotted : 3 Hours

Full Marks : 70

*The figures in the margin indicate full marks.
Candidates are required to give their answers in their own
words as far as practicable.*

GROUP - A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for any *ten* of the following : $10 \times 1 = 10$
 - i) The advantage of an 180° conduction three phase inverter over an 120° conduction three phase inverter is
 - a) it needs less number of switches
 - b) there is no paralleling of switches
 - c) devices in series are not simultaneously switches
 - d) load terminals are not left open during switches.

[Turn over

- ii) A freewheeling diode across inductive load of a phase-controlled converter will provide
- a) quick turn-on of SCR
 - b) slow turn-off of SCR
 - c) reduced utilization factor of transformer
 - ☒ d) improved power factor.
- iii) The switching frequency of a MOSFET will be reduced with
- a) an increase in the output impedance of the device
 - b) an increase in the discharge rate of the input capacitance
 - c) an increase in the source resistance
 - d) a decrease in the discharge rate of the input capacitance.
- iv) For a two-quadrant type-A chopper, regenerative braking is
- a) possible at low speeds
 - b) possible at high speeds
 - ☒ c) possible at both high and low speeds
 - d) not possible at all.
- v) RC snubber circuit is used to limit rate of
- a) rise of current in SCR
 - b) rise of voltage across SCR
 - c) rise of capacitance of depletion layer
 - ☒ d) all of these.

- vi) RC snubber circuit is used to limit rate of
- a) rise of current in SCR
 - b) rise of voltage across SCR
 - c) conduction period
 - ☒ d) all of these.
- vii) Cyclo-converter is a
- ☒ a) AC to AC converter
 - b) AC to DC converter
 - c) DC to AC converter
 - d) DC to DC converter.
- viii) The range of firing angle in case of RC firing circuit will be <http://www.makaut.com>
- a) $0^\circ - 90^\circ$
 - b) $90^\circ - 180^\circ$
 - ☒ c) $0^\circ - 180^\circ$
 - d) $45^\circ - 90^\circ$
- ix) The output voltage waveform of a three phase square wave inverter contains
- ☒ a) only odd harmonics
 - b) both odd and even harmonics
 - c) only even harmonics
 - d) only triplen harmonics.
- x) A 1-phase full bridge VSI has inductor L as load. For a constant voltage source, the current through the inductor is
- a) square wave
 - ☒ b) triangular wave
 - c) sine wave
 - d) pulse wave.

- xi) The cyclo-converters (CCs) require
- a) Natural commutation in both step-up and step-down CCs
 - b) Forced commutation in both step-up and step-down CCs
 - c) Forced commutation in step-down CCs
 - d) Forced commutation in step-up CCs.
- xii) Compared BJT, MOSFET has
- a) low switching frequency and low conduction loss
 - b) high switching frequency and low conduction loss
 - c) high switching frequency and high conduction loss
 - d) low switching frequency and high conduction loss.

GROUP - B

(Short Answer Type Questions)

Answer any *three* of the following. $3 \times 5 = 15$

2. Describe the effect of source inductance on the output voltage of a single phase full controlled bridge converter.

3. What is snubber circuit ? Why snubber circuit are used in thyristor circuit ? 3 + 2

4. Briefly describe the working of class B chopper with diagram.
5. A thyristor is used to feed a load resistance 8 ohms from a 230 V single phase supply. The ratings of thyristors are repetitive peak current = 200 A, $(di/dt)_{max} = 40 \text{ A}/\mu\text{s}$ and $(dv/dt)_{max} = 150 \text{ V}/\mu\text{s}$. Design a snubber circuit for protection of thyristor.
6. What is cyclo-converter ? Explain the operation of a single phase step-up cyclo-converter.

GROUP - C

(Long Answer Type Questions)

Answer any *three* of the following. $3 \times 15 = 45$

7. a) Describe the different modes of operation of thyristor using static V-I characteristics. What is the effect of gate current on this characteristic ?
- b) With two transistor analogy explain how a small gate current can turn-on a SCR.
- c) What is the necessity of connecting SCRs in series ? What are the problem associated with series connection of SCRs ? How are they eliminated ?

5 + 5 + 5

8. a) What is the difference between semi converter and full converter ?
- b) A single-phase fully controlled bridge converter is supplied from 230 V, 50 Hz ac supply and fed to a load which consists of $R = 20 \Omega$ and large inductance, so that load current is constant and ripple free. If the firing angle is 30° find the
- i) average and rms of load voltage
 - ii) average and rms of thyristor current
 - iii) average and rms of source current and
 - iv) input power factor. <http://www.makaut.com>
- c) A three-phase half wave-controlled rectifier connected across R load. Draw the output voltage and phase current waveforms. And also find out the expression of average output voltage at a firing angle of α $\left[\text{where, } 0 < \alpha < \frac{\pi}{6} \right]$. 2 + 8 + 5
9. a) Derive the expression for ripple of inductor current for dc to dc buck converter. And also find out the value of duty cycle at which the ripple will be maximum.

- b) Draw and explain a DC-DC boost converter. Derive an expression for average output voltage.
- c) A step-down chopper has a resistive load of $R = 10 \Omega$ and input voltage of 120 V. when the chopper is turned on, its voltage drop is 2 V. The chopper frequency is 1 KHz. If the duty cycle is 40% determine

i) Average output voltage

ii) RMS output voltage

iii) Efficiency of chopper.

4 + 5 + 6

10. a) State the comparison between voltage source inverter (VSI) and current source inverter (CSI).

b) Draw the appropriate circuit diagram of three-phase bridge inverter connected to star connected resistive load and explain the operation with the help of phase voltage, line voltage and gate pulse waveforms for 120° conduction mode.

c) A three-phase inverter is supplied from a 580 V source. For a star connected resistive load of 20Ω per phase, for 120° conduction. Determine the

i) rms value of phase voltage

ii) rms value of thyristor current.

2 + 9 + 4

[Turn over

CS/B.TECH/EE/EVEN/SEM-6/EE-603/2018-19

11. Write short notes on any *three* of the following : 3×5

- a) Turn on methods of thyristor
- b) Complementary commutation
- c) Effect of source inductance for 2-pulse converter
- d) Sinusoidal PWM
- e) Schottkey barrier diode
- f) Two-Quadrant chopper.

=====

<http://www.makaut.com>

Whatsapp @ 9300930012

Your old paper & get 10/-

पुराने पेपर्स भेजे और 10 रुपये पायें,

Paytm or Google Pay से