

© NBT Tech Add/Sem 1/F.S-181/2014-15

ES-101

## **BASIC ELECTRICAL AND ELECTRONICS ENGINEERING**

Figure A Heated: 1 Hours

Page Marks 70

The questions are of equal value  
The figures in the margin indicate full marks.  
Candidates are required to give their answers in their own words as far as practicable

## PART - I (Electrical)

(Use blue colour answer book for this part)

**GROUP A**


**(Multiple Choice Type Questions)**

Answer any five questions 5 x 1 = 5

- (i) Force experienced by a small conductor of length L, carrying current I, placed in a magnetic field B, is at an angle  $\theta$  with respect to B is given by  
 (A)  $BI$       (B)  $BI\sin\theta$       (C)  $BI\cos\theta$       (D) zero



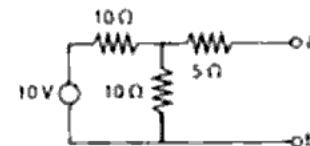- (iii) For the circuit shown the Thevenin's voltage and resistance as shown at ab are



- (A) 5 V, 10 ohm      (B) 10 V, 10 ohm    (C) 5V, 5 ohm      (D) 15 V, 15 ohm

CBSE Tech Add/Sem 1/ES-10/2014-15


- (i) Inductive reactance of a coil of inductance will be proportional to  
 (A) 62.8 ohm      (B) 628 ohm      (C) 0.2 ohm      (D) 26 ohm
- (ii) The power factor of a purely inductive will be proportional to  
 (A) zero      (B) one      (C) infinity      (D) 0.5
- (iii) The form factor current is 1, its shape is  
 (A) sinusoidal      (B) triangle      (C) square      (D) sawtooth
- (iv) The unit of mmf is  
 (A) A/m      (B) N/Wb      (C) both (A) and (B)      (D) Wbm<sup>2</sup>

**GROUP B**


## (Short Answer Type Questions)

Answer any two questions.

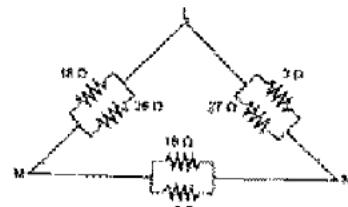2. A network of resistance is formed as given in the figure. Compute the resistance measured between L and M.



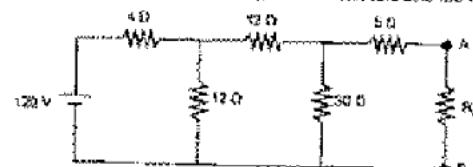3. Obtain the maximum power transferred to R<sub>2</sub> in the circuit and also the value of R<sub>2</sub>.



CBSE Tech Add/Sem 1/ES-10/2014-15

4. Two impedances  $Z_1 = (12\sqrt{3} + j(16\sqrt{3})) \Omega$  and  $Z_2 = (16 - j4) \Omega$  are connected in parallel across a 200 V, 50 Hz supply. Find the current through each impedance and total current. What is the phase difference angle of each branch current with respect to the applied voltage?
5. Derive an expression for the lifting power of an electromagnet.


**GROUP C**

## (Long Answer Type Questions)

Answer any two questions.

2+10=20

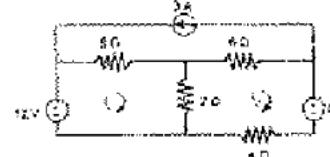6. (a) Using Mesh analysis, determine the currents I<sub>1</sub> and I<sub>2</sub> in the network shown below



- (b) Determine the voltage across 3 ohm resistor by applying Thevenin's Theorem in the following network.



7. (a) A coil of resistance 10 ohm and inductance 0.02 H is connected in series with another coil of resistance 6 ohm and inductance 15 mH across a 230 V, 50 Hz supply.

Calculate (i) impedance of the circuit

(ii) the voltage drop across each coil and

(iii) the total power consumed by the circuit

- (b) Define Power factor. Show that the active power of a purely capacitive circuit over a complete cycle is zero.

6

10+3=13


ESSP-Tech/ed1/Sep-1998-184/2016-13

8. (a) State Faraday's Laws of Electromagnetic Induction. Show that  $M = K \sqrt{L_1 L_2}$ . Where  $M$  is the mutual inductance between the coils  $L_1$  and  $L_2$ , and  $K$  is the coefficient of coupling.

(b) A coil of 250 turns carrying a current of 2A produces a flux of 0.3 mWb. When the current is reduced to zero in 2 ms, the voltage induced in a nearby coil is 60 V. Calculate the self-inductance of each coil and the mutual inductance between the two coils. Assume no coefficient of coupling to be 0.7.

9. (a) Explain Delta ( $\Delta$ ) - Star ( $Y$ ) conversion and Star ( $Y$ ) - Delta ( $\Delta$ ) conversion, for a purely resistive circuit.

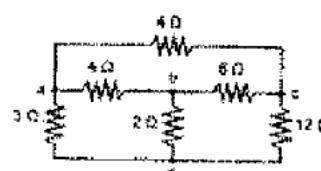(b) Redraw the network given in Fig. 1.1.1(a) as a delta connection.



Journal of Health Politics, Policy and Law, Vol. 33, No. 3, June 2008  
DOI 10.1215/03616878-33-2-491 © 2008 by the Southern Political Science Association

**PART - II (Electronics)**

*Give green color to paper back for this year*

GROUP 3

#### **Multiple Choice Type Questions**

523

CSE Tech /odd/Sem I/ES-101/2014-15

**GROUP B**  
(Short Answer Type Questions)

Answer any two questions.

2. (i) Explain the drift and diffusive current for a semiconductor.  
(ii) What is meant by intrinsic semiconductor?
3. At 300 K, the intrinsic carrier concentration of Si is  $1.5 \times 10^{16} \text{ m}^{-3}$ . If the electron and hole mobility are 0.13 and  $0.05 \text{ m}^2/\text{V}\cdot\text{s}$ , calculate the intrinsic resistivity of Si at 300 K.
4. Distinguish between zener break down and avalanche break down.

**GROUP C**  
(Long Answer Type Questions)

Answer any two questions.

5. (i) Define Fermi level.  
(ii) What is the position of Fermi level in an intrinsic semiconductor? How does its position change when (a) donors and (b) acceptors are added to the semiconductor?  
(iii) Draw the energy band diagram of a (a) forward biased pn junction diode (b) reverse biased pn junction diode (c) unbiased pn junction diode.  
(iv) Determine the resistivity of germanium (a) in intrinsic condition at 300K (b) with donor impurity of  $1 \times 10^{17}$  (c) with acceptor impurity of  $1 \times 10^{16}$ . Given that for germanium at 300K,  $n_i = 2.5 \times 10^{10} \text{ cm}^{-3}$ ,  $\mu_n = 3800 \text{ cm}^2/\text{V}\cdot\text{s}$ ,  $\mu_p = 1800 \text{ cm}^2/\text{V}\cdot\text{s}$  and number of germanium atoms /  $\text{cm}^{-3} = 4.4 \times 10^{22}$ .
6. (i) Explain the operation of a half-wave rectifier with the help of circuit diagram. Obtain a mathematical expression for the efficiency of the half-wave rectifier and show that its ripple factor is 1.23.


CSE Tech /odd/Sem I/ES-101/2014-15

- (ii) A diode having internal resistance 20  $\Omega$  is used for half-wave rectification. The ac input voltage is 6 sin  $\omega t$  and load resistance is 500  $\Omega$ . Obtain (a) dc output voltage  
(b) ac input power (c) ripple factor and (d) the efficiency of the rectifier.

7. (i) Draw the circuit diagram and output characteristics of a common emitter transistor showing different regions.

- (ii) Explain the concept of thermal run-away and Q-point.

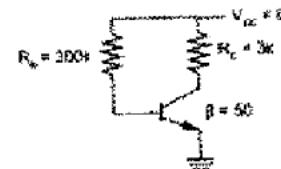- (iii) Calculate  $V_{BE}$  and  $I_C$  in the circuit below. Assume  $V_{BE} = 0.7 \text{ V}$



8. Write short notes on any two of the following:

- (a) Zener diode as a voltage regulator
- (b) Junction capacitances
- (c) Stability factors
- (d) Varactor diode