



Name :

Roll No. :

Invigilator's Signature :

CS / B.TECH (IT) / SEM-3 / EC-311/ 2010-11

2010-11

ELECTRONIC SYSTEM DESIGN

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

GROUP – A

(Multiple Choice Type Questions)

1. Choose the correct alternatives for any *ten* of the following :

10 × 1 = 10

i) A band-pass filter is narrow band if

a) $Q = 10$

b) $Q < 10$

c) $Q > 10$

d) $Q = 1$.

ii) The value of slew rate for an ideal Op – Amp is

a) 0


b) 1

c) ∞

d) less than unity.



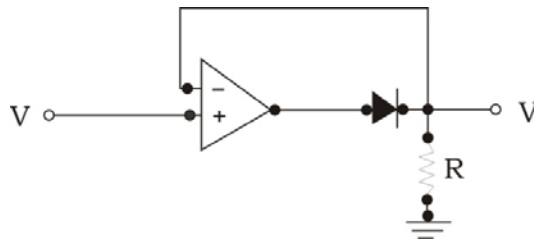- iii) An instrumentation amplifier
- a) is a differential amplifier
 - b) has a gain less than 1
 - c) has very high output impedance
 - d) has low CMRR.
- iv) The circuit which determines whether an input is between two threshold levels is called
- a) peak detector
 - b) window detector
 - c) phase detector
 - d) zero-crossing detector.
- v) The circuit shown below works as



- a) amplifier
- b) Schmitt trigger
- c) inverter
- d) halfwave rectifier.



vi) A second order high-pass filter has a roll-off rate

- a) -20dB/decade b) $+20\text{dB/decade}$
- c) -40dB/decade d) $+40\text{dB/decade}$.

vii) A Butterworth filter has


- a) flat passband, ripple stopband
- b) flat passband, flat stopband
- c) ripple passband, ripple stopband
- d) ripple passband, flat stopband.

viii) To avoid false triggering of the NE 555 timer, the RESET Pin (Pin 4) is generally connected to

- a) Pin 8 b) Pin 1
- c) Pin 3 d) No connection (NC).



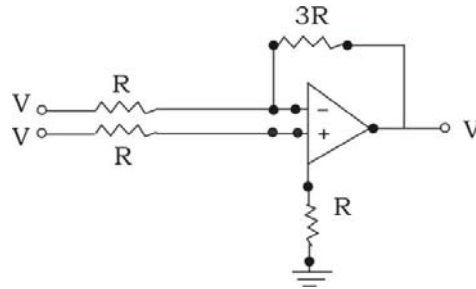ix) The value of V_0 in the figure below is



- a) $-3V_1 + 0.5V_2$ b) $-3V_2$
- c) $1.5V_2 - 2.25V_1$ d) $2V_2 - 3V_1$.
- x) Ability of an Op – Amp to provide sufficient differential mode signal but to reject the common mode signal is given by
- a) closed loop gain b) open loop gain
- c) CMRR d) PSRR.
- xi) If $A_d = 3500$ and $A_c = 0.35$, the CMRR is
- a) 1225 dB b) 10000 dB
- c) 80 dB d) both (b) and (c).



xii) In series voltage regulator the pass transistor acts as

- a) a CE-amplifier b) a CB-amplifier
- c) an emitter follower d) a switch.


GROUP – B

(Short Answer Type Questions)

Answer any *three* of the following. $3 \times 5 = 15$

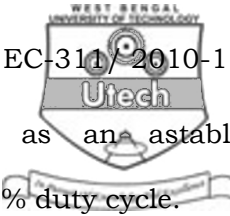2. Draw the circuit diagram and explain the operation of the window comparator.
3. Define the following electrical parameters :

Input bias current, input offset current, input offset voltage, CMRR and slew rate.
4. Draw the circuit of a voltage to current converter if the load is (i) floating and (ii) grounded. Is there any limitation on the size of the load when grounded ?
5. Explain how to get the square and square root of a given analog signal.



6. Explain the operation of 555 timer as an astable multivibrator producing the waveform of 50% duty cycle.

GROUP – C

(Long Answer Type Questions)

Answer any *three* of the following. $3 \times 15 = 45$

7. Draw the circuit of a lowpass second order active filter. Analyze the circuit and derive the gain-frequency relation. Design the circuit for gain 2 and cut-off frequency 1 kHz.
8. Set up a computer simulation to solve the differential equation, $d^2v/dt^2 + 2v - 5\sin \omega t = 0$,

where, $v(0) = -1, dv/dt = 0$ at $t = 0$.
9. Draw the circuit of an Instrumentation Amplifier and derive the expression of voltage gain. With the help of a transducer bridge how do the instrumentational amplifiers monitor the environmental change ?
10. Draw and explain the Wien-bridge oscillator circuit. Find out the expression for the operating frequency.



11. Write short notes on any *three* of the following :

- i) Phase Shift Oscillator
- ii) Log Amplifier
- iii) Differentiator
- iv) Square wave generator.

=====