

Name : .....

Roll No. : .....

Invigilator's Signature : .....

**CS/M.Tech(AEIE)/SEM-1/EIEM-101/2012-13**

**2012**

**ADVANCED ELECTRONIC CIRCUITS**

Time Allotted : 3 Hours

Full Marks : 70

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words as far as practicable.*

Answer any *five* Questions.

*All questions carry equal marks :*

1. a) Find out the relationship between output current and reference current of a Widlar current source. 9  
b) Utilizing a reference current of  $100 - \mu\text{A}$ , design a Widlar current source to provide an output current of  $10 \mu\text{A}$ . Let the BJT have  $V_{BE} = 0.7 \text{ V}$  at  $1\text{-mA}$  current assume  $\beta$  to be high. 5
2. a) Explain with the help of a diagram the operation of an active loaded MOS differential pair. 5  
b) Determine the transconductance  $G_m =$  and CMRR of the above MOS differential pair. 9
3. a) The BJT in the following circuit (Fig.-1) has  $V_{BE}=0.7 \text{ V}$   $\beta = 200$  and  $V_A -100 \text{ V}$  Find  $R_0$ . 6  
b) Derive an expression for the output resistance of cascode MOS mirror. 8
4. a) What is a phase-locked loop ? Illustrate its working principle with the help of a simplified block diagram. 5  
b) Define loop locked range. Making use of detailed block diagram derive an expression for loop locked range. 9



5. a) What is propagation delay of a CMOS inverter? Derive an expression for  $t_{PHL}$  of an inverter. 9
- b) A CMOS inverter for which  $K_n = 10 K_p = 100 \mu A/V^2$ , and  $V_t = 0.5 V$  is connected to a sinusoidal signal source having Thevenin equivalent voltage of  $0.1 V$  peak amplitude and resistance of  $100 k\Omega$ . What signal voltage appears at the output of the inverter with  $V_1 = +1.5 V$ ? 5
6. a) Illustrate the use of hysteresis in the comparator characteristics as a means of rejecting interference. 7
- b) A bistable circuit is derived from a positive feedback loop by applying  $V_1$  through  $R_1$ . Let  $L^+ = L^- = 10 V$  and  $R_1 = 1 k\Omega$ . Find the value of  $R_2$  that gives a hysteresis of  $100mV$  width. 7
7. a) Explain giving suitable diagram the operation of a CMOS SRAM. 7
- b) Draw the relevant parts of the SRAM cell during a read operation. 7
8. a) Describe the operation of ECL 10k logic family as shown in Fig.-2. 9
- b) Calculate the value of  $V_R$  generated in the temperature and voltage compensated bias network in Fig.-2. 5
9. a) Obtain an expression for differential input resistance ( $R_{id}$ ) of a general purpose 741 op-amp. If  $\beta_N$  of npn transistor is 200 and bias current is  $9.5 \mu A$ , find the value of  $R_{id}$ . 8
- b) Also find the value of output resistance ( $R_o$ ) of the 741 op-amp. 6

 


Fig.-1

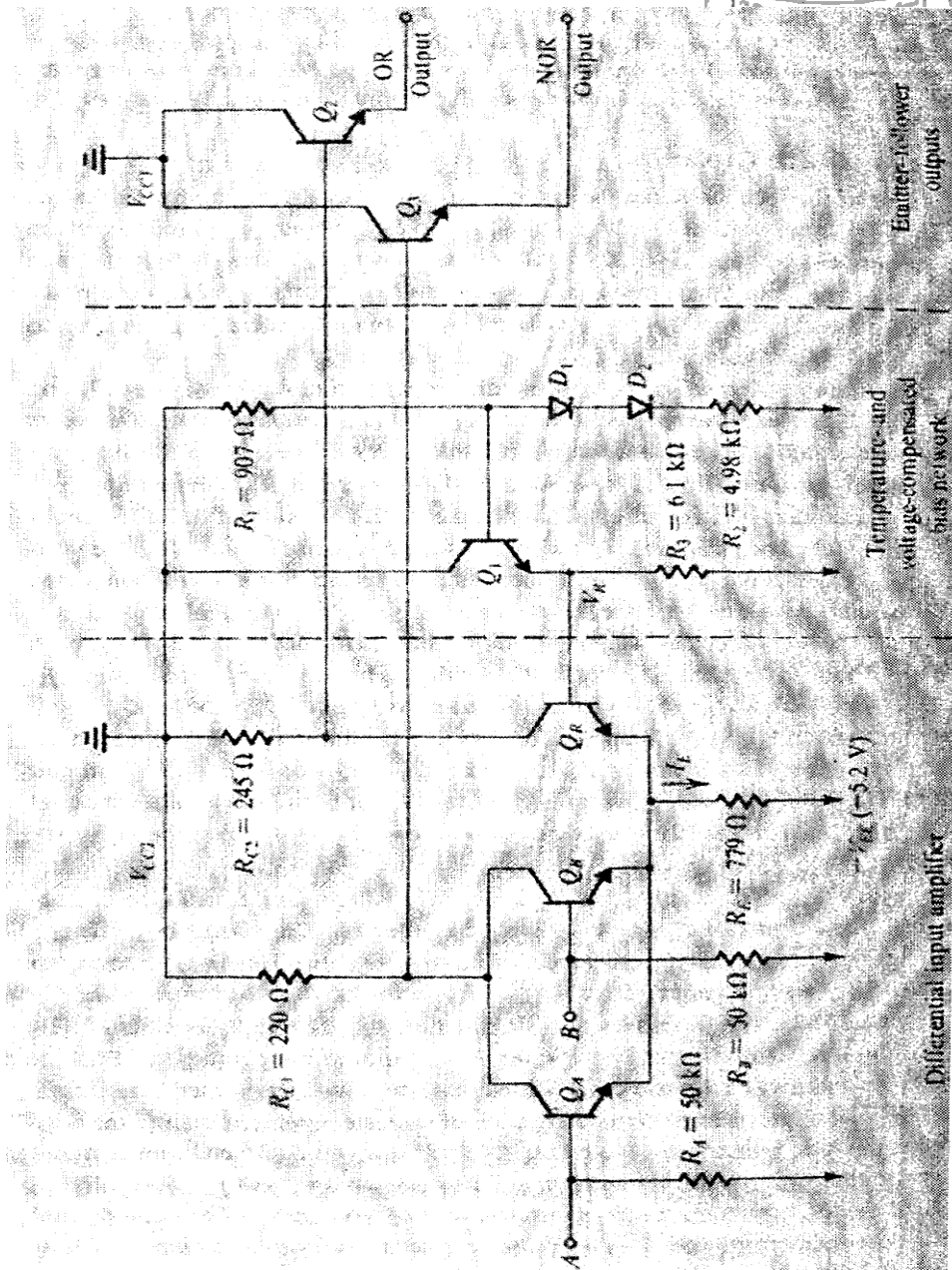


Fig.-2