



Name :
Roll No. :
Invigilator's Signature :

CS/M.TECH(ECE-VLSI)/SEM-1/MVLSI-103/2011-12

2011

DIGITAL IC DESIGN

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

GROUP – A

(Short Answer Type Questions)

1. Answer *all* the following questions :
 - i) Distinguish between dual and complement of switching function. Find the dual and complement of $F = A (B + C)$.
 - ii) Distinguish between ratioed and ratioless inverter.
 - iii) Define V_{IL} , V_{IH} , V_{OL} and V_{OH} of an inverter.
 - iv) N-MOS is good in passing a '0' and P-MOS is good in passing an '1' — justify.
 - v) Describe VHDL programming of full adder using behavioural modeling style. 2 + 3 + 2 + 3 + 4



GROUP – B

(Long Answer Type Questions)

Answer any *four* of the following.

4 × 14 = 56

2. What do you mean HDL ? How many hardware modeling present in VHDL ? Briefly discuss with proper example of various hardware modeling in VHDL. What do you mean by Top down design and Bottom up design style ? 1 + 1 + 8 + 4
3. What is meant by Domino Logic ? Design Domino Circuit with output $F = A' + B'C$. 6 + 8
4. Explain the principle of working of Transmission Gates. Realize the following function using Transmission Gate :
 $F = AB + BC + C'$ 6 + 8
5. Why we need CAD tools ? Briefly discuss about Placement, Floor planning and Routing. Why they need ? Draw the figure of PLA, where, $F_1 = xy + x'z$; $F_2 = y' + x'z$ and $F_3 = xy + y'z$. 1 + 8 + 5
6. Explain the advantages of CPL over Transmission Gates. Draw a neat diagram of a CPL based XOR gate and explain its working with particular reference to the level restoring PMOS gates. 4 + 10
7. What are VLSI design cycle and Physical design cycle ? Briefly describe about digital design process in CAD tools. 7 + 7

=====