



Name :
Roll No. :
Invigilator's Signature :

CS/M.TECH (ECE)/SEM-3/MVLSI-302/2011-12

2011

ANALOG & DIGITAL VLSI CIRCUIT & SYSTEMS

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

GROUP – A

(Objective Type Questions)

1. Answer any *five* questions : $5 \times 2 = 10$
 - a) The odd no. of inverter forms a close loop with positive feedback (ring oscillator), whose frequency of oscillation is
 - b) If $K_n = 3K_p$, then what is the ratio of $(W/L)_p$ and $(W/L)_n$ to make $\beta_n = \beta_p$?
 - c) For n input NAND gate driving a capacitance load C_L , what is the approximate expression of rising and falling propagation delay ?
 - d) What is the minimum threshold voltage for which the leakage current through an off transistor ($V_{gs} = 0$) is 10^3 times less than that of a transistor that is barely on ($V_{gs} = V_{th}$) at room temperature if $n = 1.5$?



- e) Consider a N-MOS transistor in a 180nm process with $(W/L) = (4/2) \lambda$ (0.36/0.18). In this process the gate oxide thickness is 40 angstrom and the mobility of electron is $180 \text{ cm}^2/\text{V sec}$ at 78°C temperature. The threshold voltage is 0.4V. Plot I_d vs V_{ds} graph for $V_{gs} = 0, 0.3, 0.6, 0.9, 1.2, 1.5, 1.8\text{V}$.
- f) For a high-pass passive RC filter, derive its gain and phase angle and plot it properly.
- g) What are the caveats of Miller's theorem ? Explain it with examples.

GROUP – B

(Short Answer Type Questions)

Answer any *three* questions : $3 \times 5 = 15$


- 2. What are the reduction and concatenation operators in Verilog ? Explain with examples.
- 3. What are the different data types in Verilog ? Explain different net data types of wire.
- 4. What is logical effort ? Describe the relation between normalized delay(d), logical effort(f), electrical effort(h) and parasitic delay(p) $d = f + hp$.
- 5. What is back gate effect in MOSFET ? Express g_{mb} in terms of g_m .

GROUP – C



(Long Answer Type Questions)

Answer any *three* questions : $3 \times 15 = 45$

 
- 6. a) Write all the three equations of g_m and plot the graphs showing MOS trans-conductance as a function of overdrive voltage, drain current and W/L ratio.



  - b) Following three figures indicate the relation between DC gain $A_v(0)$, bandwidth and output swing as a function of R_d and input (both AC and DC) voltages for a resistive load NMOS inverter. From these figures give some important tradeoffs between DC gain $A_v(0)$, bandwidth and output swing and also make comments on improvement.



 - c) Design a 4 : 1 MUX using pass transistor logic with minimum no. of transistors. 4 + 6 + 5
7. a) Give the expression for calculating delay in CMOS circuit.
- b) What happens to delay if you increase load capacitance ?
- c) What happens to delay if a resistance is included at the output of a CMOS ?



- d) Draw the logical circuit of a 4:1 MUX using tri-state buffer.
- e) What are the limitations of pass transistors ?
- f) Give the logical diagram of a tri-state buffer which eliminates the problems associated with the pass transistor.
- g) Show with a diagram how a F/F that can be implemented using MUX. $2 + 2 + 2 + 3 + 2 + 2 + 2$
8. a) What is Blocking and Non-Blocking Procedural Assignments in Verilog ? If you have to model a 4-bit right-shift register using Verilog then try to design the said example using blocking and non-blocking approach with always block.
- b) Design a 4 : 1 MUX using component instantiation in Verilog where the basic building block is a tri-state buffer.
- c) What is weak-zero-passing and strong-one-element ? Discuss with examples. $7 + 6 + 2$
9. a) Sketch a 2 i/p NAND gate with transistor width chosen to achieve effective rise and fall resistance equal to a unit inverter. Compute the rising and falling propagation delay of a NAND gate driving h identical NOR gates using Elmore Delay including the resistance and capacitance in terms of R and C .
- b) What is the logical effort of 2-input XOR gate ?
- c) What is the use of delay statement in Verilog ? Is it synthesizable or not ? $9 + 2 + 4$
10. a) Design a hex to seven segment decoder Verilog code using always block.
- b) Write down the Verilog code of a 4-bit binary up counter and its test bench counterpart. $5 + 10$
