



Name :

Roll No. :

Invigilator's Signature :

CS/M.Tech(EE)/SEM-1/CI-1.5.2/2009-10

2009

ELECTRONIC DEVICES & SYSTEMS

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

Answer Question No. 1 and any four from the rest. $5 \times 14 = 70$

1.
 - i) Why CMRR should be kept very high for operational amplifier ?
 - ii) Explain slew rate for operational amplifier.
 - iii) Define Q -factor for a bandpass filter.
 - iv) What is reverse recovery time of a power thyristor ?
 - v) Why is isolation required in the gate driver circuit of an IGBT ?
 - vi) What is Signal to Noise and Distortion (SINAD) ?
 - vii) What is the function of MODEM ? 7×2
2.
 - a) Find out the amplitude and phase of the output signal from the following configuration of circuit.

$$V_{in} = 10 \sin (10^5 u t) \text{ volts}$$



- b) Show the configuration of active notch filter. What is notch-out frequency of the filter ?
3. a) For the circuit given below derive the relationship between V_{in} and V_{out} . Also state how the circuit can be used as filter and indicate the type of the filter.

$$V_{in} = V_m \sin \omega t$$

- b) Show the configuration of a bandpass filter. Define centre frequency and bandwidth of the same.
4. a) For the following amplifier derive the relationship between input and output.



- b) For the following circuit show the output waveform.

$$v_i = 10 \sin 314 t \text{ volts}$$

5. a) The following specifications are given for a dual input balanced output differential amplifier :

$$R_C = 2.2 \text{ K}, R_E = 4.7 \text{ K}, R_{in_1} = R_{in_2} = 50 \Omega.$$

$$V_{cc} = -V_{EE} = 10 \text{ V}, \beta_{dc} = \beta_{ac} = 100, V_{BE} = 0.7 \text{ V}.$$

Determine (i) voltage gain (ii) R_{in_1} , R_{in_2} and R_o .

- b) Why is input impedance required to be high for operational amplifiers. Explain with diagram.

6. a) Define latching current and holding current for a thyristor. Which current is greater ?

A thyristor with latching current of 50 mA is triggered with a $50 \mu\text{s}$ pulse for the circuit shown below. Find out the max. value of R to ensure triggering.



- b) State the conditions to commute a thyristor. Also show the VI characteristics of a thyristor in the forward and reverse zone. Also show the same for a triac indicating difference between the two.

7. Write short notes on any *four* of the following : $4 \times 3\frac{1}{2}$

- a) Resolution of an A/D converter
- b) Quantization error of an A/D converter
- c) Signal-to-Noise Ratio (SNR) of an A/D converter
- d) Sampling rate of an A/D converter
- e) Aliasing of an A/D converter
- f) Total harmonic distortion of A/D converter.

=====