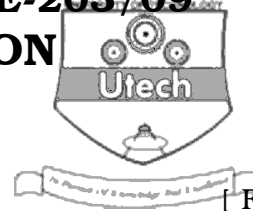


DO NOT WRITE ON THIS PAGE

CS/M.TECH (EE)/SEM-2/MEE-203/09
HVDC TRANSMISSION
SEMESTER - 2



Time : 3 Hours]

[Full Marks : 70

The figures in the margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

Answer any *five* of the following.

5 × 14 =

1. a) Compare the power transfer capacities of A.C. and D.C. transmission systems when an existing A.C. line is converted into D.C. line, with following conditions :
 - i) Same current and insulating level
 - ii) Same percentage losses and insulation level. 7

- b) A new bipolar D.C. system is compared with a three phase A.C. system. The ratio of power transmitted by D.C. to the power transmitted by A.C. is K_1 , power loss in D.C. system to the power loss in A.C. system is K_2 and A.C. line resistance is K_3 times the D.C. line resistance. If $\cos \phi$ is the power factor in A.C. system, then show that

$$\frac{\text{D.C. insulation level}}{\text{A.C. insulation level}} = 0.867 K_1 \cos \phi / \sqrt{K_2 K_3} . \quad 7$$

2. In a 6 pulse full wave converter bridge circuit with ignition angle α and commutation angle μ , find the voltage drop due to overlap and hence derive the expression of equivalent commutating resistance. 14

3. a) With neat sketches, explain the different kinds of D.C. links available. 7



- b) Obtain a relation between firing angle and power factor angle in a 3- ϕ bridge rectifier. 7
4. a) What is meant by firing angle delay, commutation delay and extinction advance angle ? 6
- b) i) A 3- ϕ , 12 pulse rectifier is fed from a transformer with nominal voltage ratings of 220 kV/110 kV. If the primary voltage is 230 kV and the effective turns ratio is 0.48, determine the *dc* output voltage when the ignition delay angle α is 20° and the commutation angle μ is 18° . 3
- ii) If the direct current delivered by the rectifier is 2,000 A, calculate the effective commutating reactance X_c , RMS fundamental component of alternating current, power factor and the reactive power at the primary side of the transformer. 5
5. a) What is MTDC system ? What are the different types of MTDC system ? 6
- b) Explain the advantages of MTDC system. 4
- c) What are the functions of DC smoothing reactor ? 4
6. Explain in detail the CIA, CEA and CC control mechanism of a simple HVDC system, What are the factors have been considered to derive the practical characteristic of RC control mechanism from ideal one ? 14
7. Write short notes on any *two* of the following : 7 + 7
- a) Commutation failure
- b) DC circuit breaker
- c) Ground return
- d) Harmonics.

END