



Name :

Roll No. :

Invigilator's Signature :

CS/M.Tech (EE)/SEM-3/PEM-301 (A)/2012-13

2012

POWER QUALITY MANAGEMENT

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

Candidates are required to give their answers in their own words as far as practicable.

Answer any *five* questions.

5 × 14 = 70

1. A distorted supply voltage $v(t)$ is applied to a load resulting a nonlinear current $i(t)$ given by the following :

$$v(t) = V_{dc} + \sum_{n=1}^{\infty} \frac{\sqrt{2}V_n}{n^2} \sin(n\omega t - \phi_{vn})$$

$$\text{with } V_{dc} = 10V, \frac{V_n}{n^2} = \frac{230\sqrt{2}}{n^2} \text{ and } \phi_{vn} = 0 \text{ for } n = 1, 3, 5, 7$$

$$\text{and } i(t) = I_{dc} + \sum_{n=1}^{\infty} \frac{\sqrt{2}I_n}{n} \sin(n\omega t - \phi_{in})$$

$$\text{with } I_{dc} = 2A, \frac{I_n}{n} = \frac{20}{n} \text{ and } \phi_{in} = n \times 30^\circ \text{ for } n = 1, 3, 5, 7$$

Compute the following :

- a) Active Power, P , Active Power related to Fundamental Component, P_1 and Active Power for Harmonic Components, P_H .



- b) Reactive Power, Q , Reactive Power related to Fundamental Component, Q_1 and Reactive Power for Harmonic Components, Q_H .
- c) Apparent Power, S , Apparent Power related to Fundamental Component, S_1 and Apparent Power for Harmonic Components, S_H .
- d) Non-active Power, N and Distortion Power, D .
- e) Displacement Power factor and Power factor.
- f) Total Harmonic Distortion (THD) of voltage and current.

3 + 3 + 2 + 2 + 2 + 2

2. A power supply has the following data :


Phase to neutral voltage = 10 kV

Short circuit level = 250 MVA

$$\frac{X_s}{R_s} = 5$$

It is supplying a star connected inductive load whose mean power is 25 kW and reactive power varies from 0 to 50 MV Ar, all quantities are on the basis of per phase.

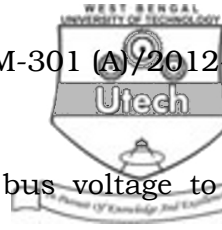- a) Find the load bus voltage and voltage drop in the supply feeder. Thus determine load current, power factor and system voltage.



- b) It is required to maintain the load bus voltage to be same as supply bus voltage i.e., $V = 10$ kV. Calculate the reactive power supplied by the compensator.
- c) What should be the load bus voltage and compensator current if it is required to maintain the unity power factor at the supply ? 4 + 5 + 5
3. a) Show that the compensator affects the no load supply voltage and voltage sensitivity of supply point voltage to the variation in the load reactive power.
- b) Consider a three-phase system with line-line voltage 11 kV and short circuit capacity of 480 MVA. With compensator gain of 100 pu determine voltage sensitivity with and without compensator. For each case, if a load reactive power changes by 10 MVar, find out the change in load bus voltage assuming linear relationship between V-Q characteristics. Also find relationship between compensator and load reactive powers. 7 + 7



4. For a star connected 3-phase, 3-wire system, 3-phase voltages are balanced sinusoids with RMS value value of 230 V at 50 Hz. The load is unbalanced and star connected and load impedances are $Z_a = 3 + j4\Omega$, $Z_b = 5 + j12\Omega$, $Z_c = 12 - j5\Omega$. Compute the following :
- a) The line currents
 - b) The active (P) and reactive (Q) powers of each phase.
 - c) The compensator susceptances so that the supply sees the load balanced and unity power factor.
 - d) For case (c), compute the source, load, compensator active and reactive powers (after compensation).
- 3 + 3 + 4 + 4
5. a) Draw the schematic of Voltage Source Inverter compensator and explain its working.
- 6 + 8
- b) Develop a state space model of the compensator.
6. a) What are the components of a DVR System ? Show a scheme for a DVR.




- b) With suitable schematic diagram explain the working of DVR based compensation in a distribution system. 7 + 7

7. Consider a system with supply voltage $230 \text{ V} = 1.0 \text{ pu}$, 50 Hz as shown in the Figure given below and feeder impedance as $Z_s = 0.05 + j 0.3 \text{ pu}$ and load impedance $Z_l = 0.5 + j 0.3 \text{ pu}$.


- a) Compute the load voltage without DVR.
b) Compute the current and DVR voltage such that $V_l = V_s$
c) Compute the effective source voltage including DVR.

Explain the power flow in the circuit.

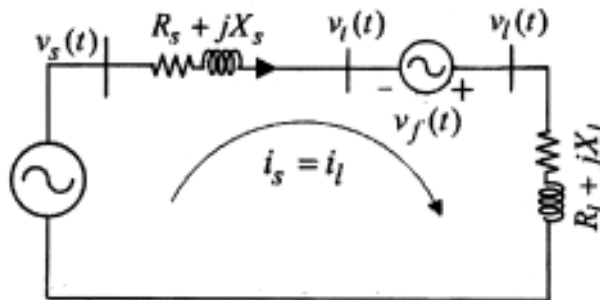- d) Compute the terminal voltage with DVR compensation.



3 + 3 + 4 + 4

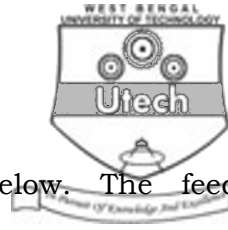


8. A DVR is shown in Figure given below. The feeder impedance of the line is $0.1 + j0.5$ pu.

Assume i_h to be load current represented by square waveform approximated by the following expression :

$$i_h = 1.0 \sin(\omega t - 30^\circ) + 0.3 \sin(3\omega t - 90^\circ) \text{ pu}$$

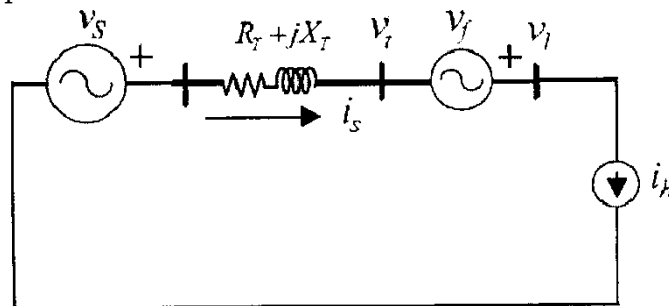- Find the load voltage $v(t)$ without DVR compensation i.e., $v_f = 0$
- Is it possible to maintain load voltage, V_l to be 1.0 pu sinusoidal waveform ? If yes what is the DVR voltage, $v_f(t)$?
- If no, how much maximum voltage can be maintained at load terminal with the DVR without taking any real power from the dc bus ?



4 + 5 + 5



9. Write short notes on any *four* of the following : $4 \times 3 \frac{1}{2}$

- a) Power factor and its correction using compensator
 - b) Improvement of voltage regulator using compensator
 - c) Scheme for Realization of DVR voltage using VSI
 - d) Theory of Instantaneous symmetrical component
 - e) Power Quality.
-