



Name : .....

Roll No. : .....

Invigilator's Signature : .....

**CS/M.Tech(EIE)/SEM-1/EIEM-101(A-3)/2009-10  
2009**

**ADVANCED ELECTRONIC CIRCUITS**

Time Allotted : 3 Hours

Full Marks : 70

*The figures in the margin indicate full marks.*

*Candidates are required to give their answers in their own words  
as far as practicable.*

Answer any *five* questions.

5 × 14 = 70

1. a) Obtain an expression for output current of a Wilson current source. What is the output resistance of the source ? 10
- b) For the Wilson current source as above the transistor parameters are  $V_{BE} = \text{cond} = 0.7V$ ,  $\beta = 50$  and  $V_A = \infty$ . For  $I_{REF} = 0.50 \text{ mA}$ . Determine the current as shown in your diagram. 4
2. a) In what respect does a CMOS op. amplifier differ from a 741 bipolar op. amp. Internal circuit diagram of a CMOS op. amp. MC14573 is enclosed ( Fig.-1 ) for the following purposes :
  - i) Explain the working principle of the various stages
  - ii) Derive expressions for reference and input stage bias currents. 10
- b) Determine the  $I_{REF}$  current in the above op. amp. if
$$\frac{1}{2} \mu_n e_{ox} = 20 \mu A/V^2 ; \quad \frac{1}{2} \mu_p e_{ox} = 10 \mu A/V^2$$
$$|V_{threshold}| = 0.5V ; V^+ = 5V ; V^- = -5V$$
and  $R_{set} = 225 \text{ k}\Omega$  4



3. a) Enclosed ( Fig. 2 ) is the internal circuit diagram of a 741 op.amp. Identify the output stage of this op. amp. and make an analysis of the same for the following parameters :
  - i) the output voltage limits
  - ii) the output resistance. 11
- b) Explain the short circuit protection mechanism provided for the output stage. 3
4. a) Make an analysis of propagation delay in a CMOS inverter and obtain an expression for  $t_{PHL}$  in terms of circuit parameters. 10
- b) Write an expression for  $t_{PLH}$  by analogy to the  $t_{PHL}$  and make at least three ( 3 ) useful observations for design. 4
5. a) Draw the basic structure of a dynamic MOS logic circuit and explain its operation using suitable waveform of the clock needed to operate the circuit Implement the logic  $Y = \overline{A + BC}$  using the above circuit. 10
- b) What are the various sources of non-ideal effects of dynamic logic circuit ? Discuss any *one* of them. 4
6. a) What is an analog switch and what are its desirable characteristics ? 4
- b) Draw the circuit diagram of a CMOS transmission gate and explain its operation. Show the equivalent circuit for the operation when analog signal is positive. 10



7. a) Draw the circuit diagram of a CMOS implemented SR-flip-flop and explain its operation. 11
- b) State the assumptions based on which flip-flop switching is predicted. 3
8. a) What are the advantages of a BiCMOS inverter over a CMOS inverter ? Explain giving circuit diagram the basic concept of a BiCMOS inverter that incorporates bleeder resistors.
- b) Make an approximate estimate of the propagation delay of a BiCMOS inverter. 14
9. Write short notes on any *two* of following : 2 × 7
- a) Widlar current source
- b) Folded cascade CMOS circuit
- c) Sense amplifier
- d) Charge – redistribution converter.

Dia.

Fig.-1 MC14573 CMOS op-amp equivalent circuit

CS / M.Tech(EIE) / SEM-1 / EIEM-101(A-3) / 2009-10



Dia.

Fig.-2

