



Name :

Roll No. :

Invigilator's Signature :

CS/M.Tech (ME)/SEM-1/ME-105/2011-12

2011

**SIGNAL CONDITIONING AND DATA ACQUISITION
SYSTEM**

Time Allotted : 3 Hours

Full Marks : 70

The figures in the margin indicate full marks.

*Candidates are required to give their answers in their own words
as far as practicable.*

Answer any five questions.


5 × 14 = 70

1. a) Why impedance matching is important in signal conditioning ? Explain with an example.

 
b) Consider a sensor having I/O relationship as

$$V_{out} = V_0 \exp (-\alpha \cdot V_{in}) \text{ where } V_0 \text{ and } \alpha \text{ are constants.}$$

How can linear I/O relationship be obtained using proper signal conditioning ?




 - c) The divider circuit, as shown in figure given below has $R_1 = 5k\Omega$ and $V_s = 5V$. Suppose R_2 is a sensor whose resistance varies from 2Ω to $4k\Omega$ as some variable varies over a range. Find (i) the minimum and maximum of V_D , (ii) the range of output impedance and (iii) the range of power dissipated by R_2 .



4 + 3 + 7

 2. a) What is 'lead compensation' ? Draw and explain a signal conditioning circuit that can be used to achieve lead compensation.
 - b) A bridge circuit is used with a sensor located 100 m away. The bridge is not lead compensated and the cable to the sensor has a resistance of $0.45\Omega/m$. The bridge nulls with $R_1 = 3400\Omega$, $R_2 = 3445\Omega$ and $R_3 = 1560\Omega$. What is sensor resistance ?
 - c) Draw and explain the 'span' and 'zero' adjustment network.
- 5 + 5 + 4
3. a) What is notch out frequency ? Write down its expression. Design a notch filter for 50 Hz power line frequency rejection.



- b) A measurement signal has frequency of $< 1\text{ kHz}$, but there is unwanted noise at 1 MHz . Design a low pass filter that attenuates the noise to 1% . What is the effect of measurement signal at its maximum of 1 kHz ?
- c) Draw and explain a voltage to current converter circuit with grounded load. 5 + 5 + 4
4. a) Draw and explain the circuit of an 'Instrumentation Amplifier'. Mention its advantages.
- b) A sensor outputs a voltage ranging from -2.4 to -1.1 V . For interface to an analog to digital converter this needs to be $0 - 2.5\text{ V}$. Design the signal conditioning circuit using 'Instrumentation Amplifier'.
- c) What is 'ladder diagram' in relation with PLC ? Draw a ladder diagram for a motor having the following conditions.
- The motor starts when the *NO* 'start' push button is pressed. A green light will glow at that time. The motor will run till *NC* 'stop' push button is pressed. When the 'stop' push button is pressed, the motor will stop and a red light will glow. 4 + 5 + 5
5. a) What type of ADCs are used for DAS and why ?
- b) Draw and explain a Multichannel DAS with parallel conversion scheme. Mention its advantages.
- c) Why sample and hold circuit is necessary with ADC ? Draw and explain the operation of switched *OP-AMP* based sample and hold circuit. Mention its advantages.


2 + 5 + 7



6. a) Draw a $R-2R$ ladder circuit of n bit DAC and prove that analog output voltage is equal to

$$V_o = -\frac{V_{ref}}{2^N} \cdot \frac{R_f}{3R} (2^{n-1}b_{n-1} + 2^{n-2}b_{n-2} + \dots + 2^1b_1 + 2^0b_0)$$

 - b) Determine the output voltage of the circuit as shown in the figure, when digital inputs are 1001 and 1101.



- c) What is the percentage resolution of 4 bit DAC ?

$$8 + 4 + 2$$

7. a) Write the difference between MUX and DEMUX with examples.

- b) Design 16 : 1 multiplexer using

- (i) 2 : 1 MUX,
- (ii) 4 : 1 MUX and
- (iii) 8 : 1 MUX.

- c) Implement the Boolean function

$$F(A, B, C, D) = \sum(0, 1, 4, 5, 9, 10, 14, 15) \text{ using multiplexer.}$$

$$4 + 6 + 4$$

8. Write short notes on any *two* of the following :

$$7 + 7$$

- a) Dual slope Integration ADC
- b) Successive approximation ADC
- c) Characteristics of DAC
- d) Data logger.

=====